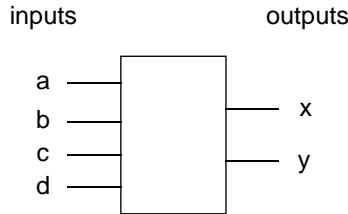


Basic Combinational Circuit

■ A combinational circuit

- Maps a set of inputs to a set of outputs
 - These inputs / outputs are called *signals*
 - Each signal has the value 1 or 0



- Whenever the input values change, the output values change after a short delay (called the *propagation delay*)
- Is purely functional
 - Output values depend only on inputs
 - There is no concept of *state* in a combinational circuit

1

Fall 1998, Lecture 05

Truth Tables

- A truth table specifies *what* a logic circuit does, but not *how* it does it
 - It lists, for every possible combination of input values, the output value(s)

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

- Our goal is to build the digital circuit that implements this truth table

2

Fall 1998, Lecture 05

Boolean Operations

- In Boolean algebra, variables assume one of two logical values:

- True = 1
- False = 0

- Boolean algebra has three basic operators:

- *and*, denoted as \cdot (sometimes omitted)
- *or*, denoted as $+$
- *not* (or *complement*, or *inversion*), denoted as $'$ or $\bar{\quad}$

- A *gate* is an electronic device that implements a simple Boolean operation

- Gates are the basic building blocks of a digital circuit

3

Fall 1998, Lecture 05

4 Basic Boolean Operations & Gates

	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>$a \cdot b$ (or ab)</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	$a \cdot b$ (or ab)	0	0	0	0	1	0	1	0	0	1	1	1	
a	b	$a \cdot b$ (or ab)															
0	0	0															
0	1	0															
1	0	0															
1	1	1															
<i>or</i>	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>$a + b$</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	$a + b$	0	0	0	0	1	1	1	0	1	1	1	1	
a	b	$a + b$															
0	0	0															
0	1	1															
1	0	1															
1	1	1															
<i>xor</i>	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>$a \oplus b$</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	a	b	$a \oplus b$	0	0	0	0	1	1	1	0	1	1	1	0	
a	b	$a \oplus b$															
0	0	0															
0	1	1															
1	0	1															
1	1	0															
<i>not</i>	<table border="1"> <thead> <tr> <th>a</th> <th>\bar{a} (or a')</th> </tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	a	\bar{a} (or a')	0	1	1	0										
a	\bar{a} (or a')																
0	1																
1	0																


4

Fall 1998, Lecture 05


Generalized Gates

- These gates can also be generalized to an arbitrary number of inputs

a	b	c	$a \cdot b \cdot c$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

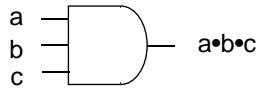

a	b	c	$a+b+c$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

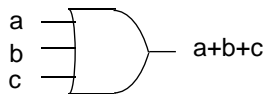


5

Fall 1998, Lecture 05

Building Combinational Circuits

- Consider the 4-input Boolean expression:
 $z = ((a'bc \oplus c) + a + d)'$

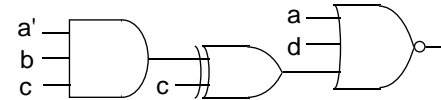- The equivalent circuit (logic) diagram would be:



Conventions in drawing logic diagrams:

- Inputs go on the left, outputs on the right
- Simplify inputs and outputs: don't show inverters
- Signal lines are drawn in rectangular fashion (i.e., no diagonals, no curves)
- It's OK for signal lines to cross; but if signal lines merge / split, indicate the junction with a black dot

6

Fall 1998, Lecture 05

Boolean Algebra

- The 10 fundamental properties are:

- commutative*

$$x + y = y + x \quad x \cdot y = y \cdot x$$

- associative*

$$x + (y + z) = (x + y) + z$$

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

- distributive*

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

- identity*

$$x + 0 = x \quad x \cdot 1 = x$$

- complement*

$$x + x' = 1 \quad x \cdot x' = 0$$

- Each property has a *dual* property, created by:

- Exchanging + and ·
- Exchanging 1 and 0

7

Fall 1998, Lecture 05

Boolean Algebra (cont.)

- These postulates can be used to prove a number of useful theorems:

- idempotency*

$$x + x = x$$

$$x \cdot x = x$$

- null*

$$x + 1 = 1$$

$$x \cdot 0 = 0$$

- absorption*

$$x + (x \cdot y) = x$$

$$x \cdot (x + y) = x$$

- De Morgan's law*

$$(x + y)' = x' \cdot y'$$

$$(x \cdot y)' = x' + y'$$

- other complement theorems*

$$(x')' = x$$

involution

$$1' = 0$$

$$0' = 1$$

8

Fall 1998, Lecture 05

2-Level Circuits

- **Every** Boolean expression can be written as **a sum of products**, and as a **product of sums**, and implemented as a 2-level circuit

$$\begin{aligned} z &= ((a'bc \oplus c) + a + d)' && \text{given} \\ &= (a'bcc' + (a'bc)'c + a + d)' && \text{defn of } \oplus \\ &= ((a'bc)'c + a + d)' && \text{complem.} \\ &= ((a+b'+c')c + a + d)' && \text{De Morg.} \\ &= (ac + b'c + a + d)' && \text{distributive} \\ &= (ac)'(b'c)'a'd' && \text{De Morg.} \\ &= (a'+c')(b+c')a'd' && \text{De Morg.} \\ &= (a'+a'c')(b+c')d' && \text{distributive} \\ &= (a'b + a'c' + a'bc' + a'c')d' && \text{distributive} \\ &= (a'b + a'c' + a'bc')d' && x+x=x \\ &= a'bd' + a'c'd' + a'bc'd' && \text{distributive} \end{aligned}$$

(this result is sum of products form)

Homework #1 — Due 9/14/98 (Part 3/3)

6. Draw the combinational circuit that directly implements the Boolean expression $a = bc'd + (b' + d)(cd')$

(This is the last question on Homework #1)