 


Constructing a Truth Table

- Given a circuit diagram, a truth table can easily be constructed:



a	b	c	d	a'bc	(a'bc) ⊕ c	((a'bc) ⊕ c) + a + d	((a'bc) ⊕ c) + a + d'
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	1	1	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	0	0	1	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	1	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	1	0
1	1	0	1	0	0	1	0
1	1	1	0	0	1	1	0
1	1	1	1	0	1	1	0



1

Fall 1998, Lecture 06

Implementing a Truth Table

- For a given truth table, there may be more than one valid implementation

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

  

2

Fall 1998, Lecture 06

Implementing a Truth Table (cont.)


- Unfortunately, there also may be more than one 2-level implementation:

$$z = a'bd' + a'c'd' + a'bc'd'$$

$$= a'bd' + (a'c'd') + (a'c'd')b$$

$$= a'bd' + a'c'd'$$

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

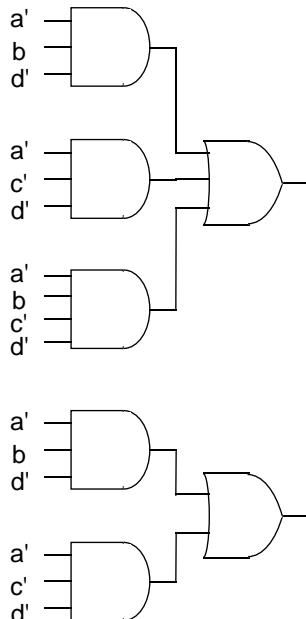


3

Fall 1998, Lecture 06

3-Variable Karnaugh Maps


- Given a Boolean expression, we can construct a *Karnaugh map* by drawing a box as shown below and writing 1's in all the appropriate boxes whenever that term is true

$$z = a'bc + abc + ab$$

 

- Then we find the *smallest* set of ovals of size 1, 2, 4, or 8, that cover all the 1s (but none of the 0s), and write out the *minimized expression* from those ovals

$$z = bc + ab$$

 


4

Fall 1998, Lecture 06

3- Variable Karnaugh Maps (cont.)


- The ovals should be as big as possible, and two or more ovals can overlap

$$z = a + b$$

 

- Ovals can even wrap around the ends (or top and bottom) of the table

$$z = c' + a'b'$$

 

- But ovals can't go diagonally

5



Fall 1998, Lecture 06

4-Variable Karnaugh Maps

- 4-variable Karnaugh maps are similar, but now ovals can be of size 16 as well

- Now we can finally make sure that we have the minimum 2-level *and-or* (SOP) implementation of our example:

$$z = ((a'bc \oplus c) + a + d)'$$

 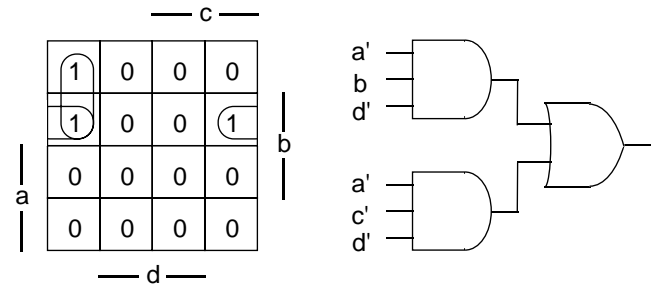

$$= a'bd' + a'c'd'$$



- Could also build Karnaugh map directly from truth table, entering a "1" in each box that corresponds to a combination of inputs that produce an output of 1

6


Fall 1998, Lecture 06

Negation / Universal Gate

  - *Nand* and *nor* gates are very easy to construct



 - Any digital circuit can be implemented using only *nand* or *nor* gates




7


Fall 1998, Lecture 06

Example from Earlier in the Lecture

- In 2-level *and-or* form:

 

- In 2-level *nand* form:

 

8

Fall 1998, Lecture 06

Homework #2 — Due 9/28/98 (Part 1)

1. Find the minimized expression that corresponds to each of the following Karnaugh maps:

	— c —			
a	1	0	0	1
a	0	1	1	0
	— b —			

	— c —			
a	1	1	1	1
a	0	1	1	0
	— b —			

2. Use a Karnaugh map to minimize the 4-variable Boolean expression
 $z = a'b + b'c + abc + abcd$