

Adders, ALUs, etc.

- In a digital circuit, there is often a need to perform arithmetic computations: addition, subtraction, multiplication, etc.
- Depending on the available functional units in the module library being used, the designer may have one or more alternatives:
 - Dedicated functional units:
 - adder
 - subtractor
 - multiplier
 - Multi-function functional units:
 - adder / subtractor
 - More general functional units = Arithmetic Logic Units (ALUs):
 - ALU (addition, subtraction, multiplication)
 - ALU (addition, subtraction, multiplication, division, comparison)

1

Fall 1998, Lecture 07

Half Adder

- Consider what happens when you add two binary digits:

$$\begin{array}{r}
 0 \\
 +0 \\
 \hline
 0) 0
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 +1 \\
 \hline
 0) 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 +0 \\
 \hline
 0) 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 +1 \\
 \hline
 1) 0
 \end{array}$$

↑ carry out
 ↑ sum

- We can construct a truth table for a *half adder* (HA) — a device that adds two binary digits a and b , producing a *sum* and a *carry out*


a	b	sum	cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

2


Fall 1998, Lecture 07

Implementing a Half Adder

 - A half adder can be implemented directly in 2-level SOP form:



 - A half adder can also be implemented using an **xor** gate:



- Which implementation is better? Why?

3

Fall 1998, Lecture 07

Which Implementation of the Half Adder is Better?

- Given this number of transistors and amount of propagation delay (in ns)

	2-input	3-input	4-input
and	6 2.4	8 2.8	10 3.2
or	6 2.4	8 2.8	10 3.2
xor	14 4.2		
nand	4 1.4	8 1.8	10 2.2
nor	4 1.4	8 1.8	10 2.2
inverter (1-input)	2 1.0		

- In SOP form, using and and or gates:

- sum = ___ transistors,
- cout = ___ transistors, total ___

- Max delay until outputs are ready = ___ ns

- In SOP form, using nand gates:


- In xor form (using a single complex gate instead of three simple gates):

4

Fall 1998, Lecture 07

Full Adder

 - A half adder is fine for the *least significant bit* (LSB) of a multi-bit number, but not the other bits



- A *full adder* (FA) adds two binary digits a and b , plus a *carry in* (from the previous digit), producing a *sum* and a *carry out*


a	b	cin	cout	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

5

Fall 1998, Lecture 07

Full Adder (cont.)

 
- A full adder can be implemented directly in 2-level SOP form:



$$\text{cout} = a \cdot \text{cin} + b \cdot \text{cin} + ab$$

$$\text{sum} = ab'cin' + a'b'cin + abcin + a'bcin'$$

 - A full adder can also be implemented by two half adders:




- Again, which implementation is better, and why? Various alternatives left as an exercise for anyone interested...

6

Fall 1998, Lecture 07

n-Bit Adder

 - An n -bit adder can now be constructed out of $n-1$ full adders, and 1 half adder



- This kind of n -bit adder is called a *ripple adder*


- Why?
- What are its limitations?

7

Fall 1998, Lecture 07

Half Subtractor

 - Consider what happens when you subtract two binary digits:



- Using the same techniques that we used to construct a half adder, we can construct a *half subtractor* — a device that subtracts binary digit b from binary digit a , producing a *difference* and a *borrow*


8

Fall 1998, Lecture 07

ALU


- Just as we can build an adder or a subtractor, we could build an adder / subtractor...

sel	f
0	a+b
1	a-b

 

- ...or a more general Arithmetic Logic Unit (ALU) capable of performing a number of arithmetic functions

s1	s0	f
0	0	a+b
0	1	a-b
1	0	a•b
1	1	a&b

 

- And we can generalize this idea to construct an n -bit ALU capable of performing whatever functions we want