

## Sequential Circuits

- For several lectures, we have studied *combinational circuits* — circuits whose output values depend only on the inputs
- Now we will study sequential circuits — circuits whose output values depend on both:
  - the inputs, and
  - the current *state* of the circuit
- The *state* of the circuit is defined by the values stored in the memory elements


- 
- With sequential circuits, we can build registers, memories, shift registers, counters, stacks, queues, etc.
  - With combinational circuits, we can build adders, ALUs, and glue logic

1


Fall 1998, Lecture 08

## A Very Simple Computer Datapath

- $temp = a + b$  (a to left input...)

 

 - $z = temp + c$  (temp to left input...)



2

Fall 1998, Lecture 08


## The D Latch (Gated D Flip-Flop)

- Inputs:

- D = data
- CK = clock

- Outputs:

- Q
- Q'

 

- Operation:

- When CK is 1, Q follows D (if D changes, Q changes also, after a short delay)
- Otherwise, Q keeps its last value

- Note that the D latch keeps its value while CK is 0 (it's a sequential circuit)


- It's a memory!!

3

Fall 1998, Lecture 08
 
## Timing Diagrams

- A *timing diagram* is a graphical representation of the signals in a circuit
  - The horizontal axis represents time
  - Vertical axis represents value of each signal:
    - A 1 is represented as a high line
    - A 0 is represented as a low line
  - The timing diagram may account for *propagation delay* — the delay through a combinational element (the amount of time it takes to execute)
- Timing diagram illustrating the operation of a D latch:




4

Fall 1998, Lecture 08
 
## Clock

- It is common for a digital system to have a *clock* signal, which repeats a 0-1 pattern at regular intervals



- The *period* is the length of time that it takes to repeat the pattern
  - The part of the pattern which has the value of 1 is called the clock *pulse*
  - The 0-1 transition is called the *rising* (or *positive*) *edge*
  - The 1-0 transition is called the *falling* (or *trailing*, or *negative*) *edge*
- Clock signals are used in *synchronous* circuits — those where events happen at predictable, regular intervals

5

Fall 1998, Lecture 08

## Can We Use a D Latch as a Register?

- Potential problem: output is unstable anytime CK is 1
- Can't use as register, since register is in a closed feedback loop — can't allow values to change while they're being used in a computation
  - Want to change register values only when computation is complete
    - Read values and compute (generating garbage output until finished)
    - At end of cycle, when result is ready, store into register
    - Must make cycle long enough to allow result to stabilize!
- Useful for holding values to transfer outside the circuit
  - OK here since we'll produce a result, and then tell outside when it's safe to read it


6

Fall 1998, Lecture 08

## The (Edge-Triggered) D Flip-Flop

### Inputs:

- D = data
- CK = clock

 

### Outputs:

- Q
- Q'

### Operation:

- When CK transitions from 0 to 1 (leading edge), Q is set to the value of D (after a short delay)
  - Otherwise, Q keeps its last value, regardless of any changes in D
- We can use  $n$  D flip-flops to build an  $n$ -bit register...


7

Fall 1998, Lecture 08

## D Latch vs. D Flip-Flop
 
### D Latch:


- When CK is 1, Q follows D (if D changes, Q changes also, after a short delay)



- Not useful in building registers
 
### D Flip-Flop:

- When CK transitions from 0 to 1 (leading edge), Q is set to the value of D (after a short delay)




- Useful as a memory element in a register

8

Fall 1998, Lecture 08

 
## Building a D Flip-Flop

- Implementation is fairly complicated to analyze...


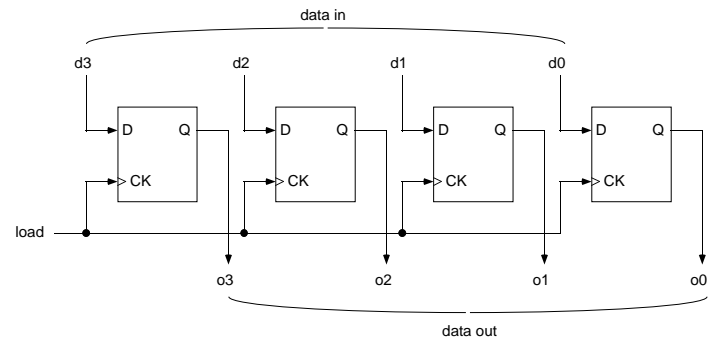
## Building a Register Out of D FFs

- This simplified diagram shows how a 4-bit register can be constructed out of 4 D flip-flops



- When the *load* signal goes high, the *data in* values (d3–d0) are stored in the register, and become available as *data out* (o3–o0) signals