

Topic 7: Combinational Circuits

Readings:


- Patterson & Hennessy Appendix B

Goals

- Boolean algebra
- Sum of products and products of sum form
- Karnaugh maps

Physical to Logical Level

4 Representations

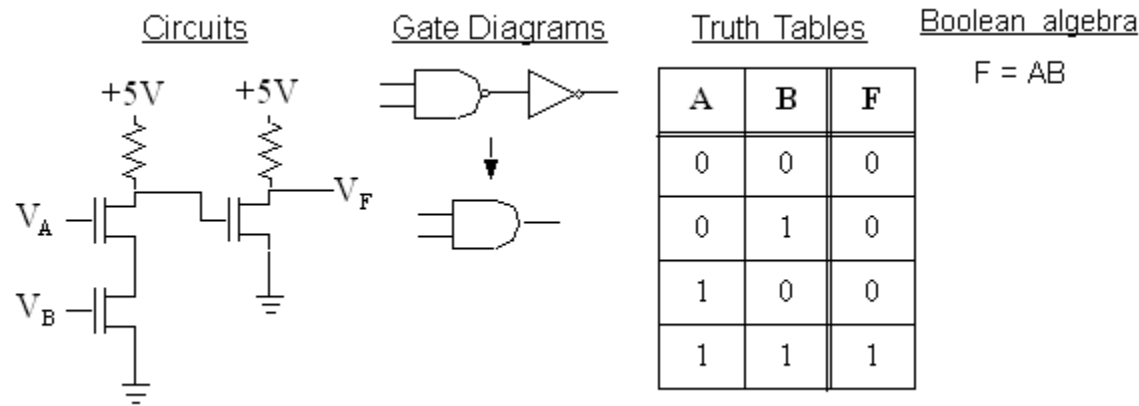

- Circuits and gate diagrams correspond one to one
- We can map gate diagrams to TTs. How about TT's into gate diagrams?

Need a tool: boolean algebra

- How to manipulate TTs ?

Translate to boolean algebra and manipulate

Boolean Algebra

Algebra: Set of Elements, Set of Functions, Set of Axioms

- Elements: $\{0,1\}$
- Functions: AND (like multiply), OR (like add), NOT (bar)

- Identities:

$$0X = 0 \quad 1 + X = 1$$

$$1X = X \quad 0 + X = X$$

- Operator Axioms

- $X\underline{X} = X \quad X + \underline{X} = X$

- $\underline{XX} = 0 \quad X + X = 1$

- AND and OR are commutative:

- $A + B = B + A \quad , \quad AB = BA$

- AND and OR obey distributive law:

- $A(B + C) = AB + AC$

- $A + (BC) = (A + B)(A + C)$

- AND takes precedence over OR

- $A + BC = A + (BC)$

- AND and OR obey associative law:

- $A + (B + C) = (A + B) + C$

- $A(BC) = (AB)C$

DeMorgan's laws

Proving Boolean Equations

Method #1: Algebraic method

$$(X + Y)(X + Z) = X + YZ$$

Method #2: Truth tables

$$(X + Y)(X + Z) = X + YZ$$

X	Y	Z	X+Y	X+ Z	LH S	YZ	RHS
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Generating Boolean Equations from Truth Tables

- Find all rows with $F=1$
- AND them together to make a product term. These are called minterms.
- OR the minterms together $F = \overline{A}BC + A\overline{B}C + ABC$

A	B	C	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\overline{A}BC$
1	0	0	1	$A\overline{B}C$
1	0	1	0	
1	1	0	0	
1	1	1	1	ABC

Boolean Equations from Truth Tables (cont.)

Another Example $F = \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}$

A	B	C	D	F	
0	0	0	0	0	$\overline{A}BCD$
0	0	0	1	1	$\overline{A}BC\overline{D}$
0	0	1	0	0	$\overline{A}B\overline{C}D$
0	0	1	1	1	$\overline{A}B\overline{C}\overline{D}$
0	1	0	0	1	$A\overline{B}CD$
0	1	0	1	0	$A\overline{B}C\overline{D}$
0	1	1	0	0	$A\overline{B}\overline{C}D$
0	1	1	1	1	$A\overline{B}\overline{C}\overline{D}$
1	0	0	0	1	$\overline{A}BCD$
1	0	0	1	0	$\overline{A}BC\overline{D}$
1	0	1	0	1	$\overline{A}B\overline{C}D$
1	0	1	1	1	$\overline{A}B\overline{C}\overline{D}$
1	1	0	0	1	$A\overline{B}CD$
1	1	0	1	0	$A\overline{B}C\overline{D}$
1	1	1	0	0	$A\overline{B}\overline{C}D$
1	1	1	1	1	$A\overline{B}\overline{C}\overline{D}$

Canonical Form

- Truth Table provides a signature for the boolean function.

Is there an equivalent algebraic signature?

Sum of Products form (SOP).

- Also known as disjoint normal form or minterm expansion.
- This is what we just did in the last two examples.

Product of Sums form (POS). AKA maxterm expansion.

- Find SOP for rows where $F=0$: Invert the entire expression, and apply De Morgan's law to get POS. Each sum is called a maxterm.

A	B	C	F		
0	0	0	0	$A+B+C$	
0	0	1	0	$A+B+\overline{C}$	$(A+B+C)(A+B+\overline{C})(A+\overline{B}+C)$
0	1	0	0	$A+\overline{B}+C$	$(\overline{A}+B+\overline{C})(\overline{A}+\overline{B}+C)$
0	1	1	1		
1	0	0	1		
1	0	1	0	$\overline{A}+\overline{B}+\overline{C}$	
1	1	0	0	$\overline{A}+\overline{B}+C$	
1	1	1	1		

Canonical Form (cont.)

A	B	C	D	F		
0	0	0	0	0	$A+B+C+D$	
0	0	0	1	1		
0	0	1	0	0	$A+B+\overline{C}+D$	
0	0	1	1	1		
0	1	0	0	1		
0	1	0	1	0	$A+\overline{B}+C+\overline{D}$	$(A+\overline{B}+C+D)(\overline{A}+B+\overline{C}+\overline{D})(\overline{A}+\overline{B}+C+\overline{D})$
0	1	1	0	0	$A+\overline{B}+C+D$	$(A+\overline{B}+C+D)(A+B+C+D)(A+\overline{B}+C+D)$
0	1	1	1	1		$(\overline{A}+\overline{B}+\overline{C}+D)$
1	0	0	0	1		
1	0	0	1	0	$\overline{A}+B+C+\overline{D}$	
1	0	1	0	1		
1	0	1	1	1		
1	1	0	0	1		
1	1	0	1	0	$\overline{A}+\overline{B}+C+\overline{D}$	
1	1	1	0	0	$\overline{A}+\overline{B}+\overline{C}+D$	
1	1	1	1	1		

Implementing SOP using only NAND gates



Why just NAND gates?

- AND gates are usually just NAND gates with an inverter.
- INVERTER can be made by wiring together inputs of NAND gates



A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

  
"Pushing a Bubble" through an AND changes it to an OR, and vice versa




Implementing SOP using only NOR gates

What goes for NAND gates, goes for NOR gates:

 - Inverters can be made by wiring gates
- OR gate is sometimes implemented as NOR plus INVERTER
- Unfortunately, circuits are not very clean



 What about POS using only NOR? $F = (B + \bar{C})(\bar{B} + C)(A + C)$



Canonical Form is not minimal form

Example:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$

$$F = A + BC$$

Question: how to find minimal form?

Finding the minimal form

Goals is to reduce the number of literals in a boolean equation.

A literal is a variable and its complement in an equation.

- A1: Use Boolean Algebra. Hard to know when you're "done."
- A2: Use Karnaugh maps

Karnaugh Maps

Graphical way to unify terms

Example #1: $F = A\bar{B} + AB$

		A	
	B		
		0	1
0		0	2
1		1	3

More Karnaugh Maps

Example #2: $F = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$

C \ AB		A			
		00	01	11	10
0	0	0	2	6	4
	1	1	3	7	5


B

Goal:

- circle as few rectangles of 1's as possible, covering all 1's
- but: rectangle sides must be power-of-two in size
(e.g., 1x1, 1x2, 2x2, 1x4, 2x4, 4x4)

More Karnaugh Maps

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

 

Rules of thumb for finding minimal expressions



Suppose I have this K-Map

CD \ AB		A			
		00	01	11	10
D	00	0 0	4 1	12 0	8 0
	01	1 0	5 1	13 1	9 1
	11	3 1	7 1	15 1	11 0
	10	2 0	6 0	14 1	10 0

- Largest subcube to smallest?
- Smallest subcube to largest?

5 and 6 variable K-maps

Just a stack of 4-var K-maps

  

Mapping real problems to boolean equations





"Design a circuit for a digital clock that computes the next hour on its output, given the current hour as input."

Assumption: Hours are represented as 4 bit binary number

A	B	C	D	A'	B'	C'	D'
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	0	0	0	0
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X


Digital Clock Example

Karnaugh
Maps:

 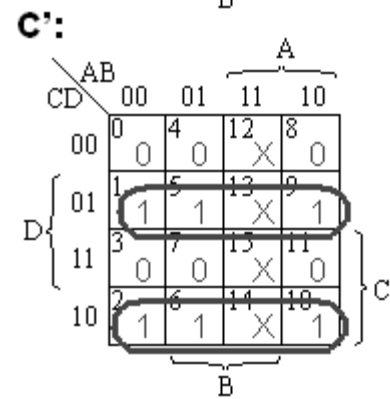  

not the
best!

Digital Clock Circuit

 

Summary

