

## CMOS Transistor Notation

- A CMOS transistor has 3 terminals, called the *gate*, *source*, and *drain*
- $V_{AB}$  is the voltage between nodes A and B in a circuit
- Positive power supply (power source)
  - In TTL, written  $V_{CC}$  (usually written VCC)
  - In NMOS and CMOS, written  $V_{DD}$  (also VDD)
- Negative power supply (power sink)
  - In TTL, written GND (“ground”)
  - In NMOS and CMOS, sometimes written  $V_{SS}$  (also VSS)
- CMOS uses positive logic:  $V_{DD}$  is logic “1”,  $V_{SS}$  is logic “0”

1

Spring 2000, Lecture 13

## CMOS Transistors as Switches

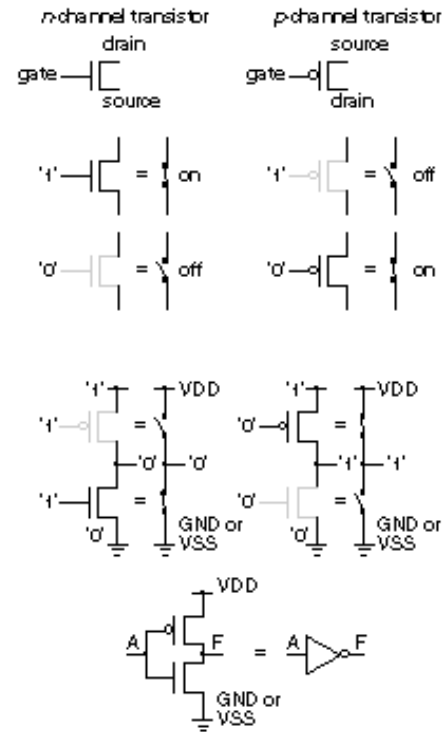


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

2

Spring 2000, Lecture 13

## CMOS NAND and NOR Gates

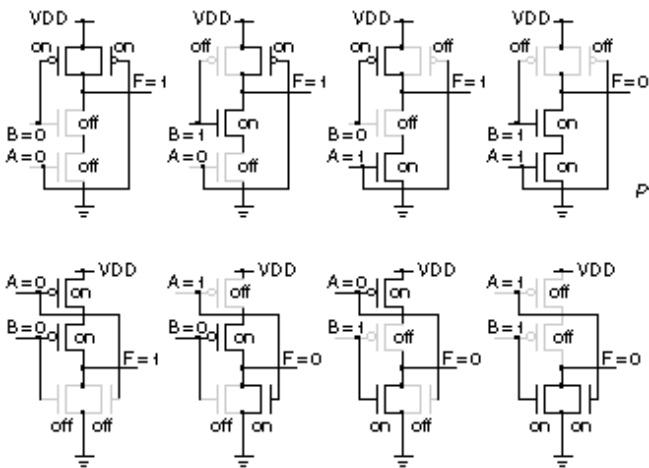


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

- Use two transistors to make a CMOS inverter (as shown on previous slide)
- Use four transistors to make a CMOS 2-input NAND gate
  - Rule of thumb: 1 gate = 4 transistors

3

Spring 2000, Lecture 13

## IC Fabrication Technologies (Implementing an Inverter)

 


Figure from *Modern VLSI Design*, Wolf, Prentice Hall, 1994

- Bipolar — transistor & resistor (**fastest**)
- NMOS — n-channel depletion mode transistor (top) & n-channel enhancement mode transistor (bottom)
- CMOS — p-channel (**lowest power**) enhancement mode transistor (top) & n-channel enhancement mode transistor (bottom)

4

Spring 2000, Lecture 13

## Cross-Section of an N-Channel Enhancement Mode MOS Transistor

 


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

- Base is silicon *substrate* (*bulk, well, tub*) that's been *doped* with p-type impurities (full of positively-charged *holes*)
  - Two *diffusion* areas heavily doped with n-type impurities (full of negatively-charged *electrons*) form the *source* and *drain*
  - Transistor action takes place at the *channel*, connecting the source and drain
- A very thin layer of silicon dioxide ( $\text{SiO}_2$ ), called the *gate oxide*, insulates the *gate*, made of polysilicon, from the channel

5

Spring 2000, Lecture 13

## Operation of an N-Channel Enhancement Mode MOS Transistor

- Works as a switch — gate-to-source voltage regulates the amount of current that can flow between drain and source
  - When  $V_{GS} = 0$ , the p-type channel is full of *holes*, and the n-type source and drain contain *electrons*
    - The p-n junctions at source and drain form *diodes* in opposite directions, so no current flows between source and drain
  - As  $V_{GS}$  rises above 0, the few n-type impurities that are present in the p-type channel start to attract electrons
    - The electrons migrate toward the (positively charged) gate, but are stopped by the gate oxide, so collect at the top of the channel
  - When  $V_{GS}$  rises to the *threshold voltage* ( $V_t$ ), enough electrons have collected to form an *n-channel inversion layer*, which allows electrons to flow from source to drain (current flows from drain to source)

6

Spring 2000, Lecture 13

## Operation of an N-Channel Enhancement Mode MOS Transistor (cont.)

- N-channel vs. p-channel
  - N-channel:  $V_{GS}$  and  $V_{DS}$  both positive, gate and source are n-type (electrons), substrate & channel is p-type (holes), when  $V_{GS} \gg V_t$  electrons accumulate in channel and flow from source to drain, current flows from drain to source
  - P-channel:  $V_{GS}$  and  $V_{DS}$  both negative, gate and source are p-type (holes), substrate & channel is n-type (electrons), when  $V_{GS} \gg$  (more negative) than  $V_t$  holes accumulate in channel and flow from source to drain, current flows from source to drain
- Current proportional to  $W/L$  of transistor
  - Length ( $L$ ) = parallel to current flow
  - As  $W$  increases, more current can flow
  - As  $L$  increases, less current flows

7

Spring 2000, Lecture 13

## Transistor Modeling

- Falling propagation delay:
 
$$t_{PDf} \approx R_{pd} (C_{out} + C_p)$$
 where:
  - $R_{pd}$  is resistance of pull-down network, proportional to  $L/W$
  - $C_{out}$  is the gate's output (extrinsic) capacitance, which depends on:
    - Wires and gates being driven
  - $C_p$  is the gate's *parasitic* (intrinsic) capacitance, which depends on:
    - Capacitance between gate and source, gate and drain, gate and substrate, source and substrate, drain and substrate
    - Hard to model; varies with  $V_{GS}$  and  $V_{DS}$
- One implication: keep transistors small
  - Related implication: keep wires short, use metal interconnections if possible
- Levels of simulation: gate, switch, timing, circuit

8

Spring 2000, Lecture 13