 


Implementing a Truth Table Using An And-Or Structure (Review)

- Given a truth table, we can use a Karnaugh map to find the minimum 2-level SOP implementation

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0



$$x = a'bd' + a'c'd'$$

1

Spring 2000, Lecture 15

PLAs

- A 2-level *and-or* structure is replicated many times in a programmable array called a *PLA (programmable logic array)*
 - Parts of a CPU's datapath or next-state logic can be built out of PLAs
 - Small circuits can be built out of PLAs
- At the input of each gate, there's a "fuse" which can be left whole, or broken
 - So the designer can control which inputs go to each and gate, and which outputs of the and gates go to each or gate
- A PLA can be either
 - Mask programmable — customer orders a programmed PLA from the manufacturer
 - Field programmable — customer can program PLA (once)

2

Spring 2000, Lecture 15

PLAs

- A 2-level *and-or* structure is replicated many times in a programmable array called a *PLA (programmable logic array)*

 


Diagram from *Computer Systems*, Maccabe, Irwin 1993

- This PLA has 2 inputs, 2 outputs, and can represent up to 3 product terms

3

Spring 2000, Lecture 15

PLA Example

- This is an *abstract* diagram of a PLA with 6 inputs, 4 outputs, which can represent up to 12 product terms

 


Diagram from *Digital Design*, Johnson & Karim, PWS-Kent 1987

- Try the Java KMap->PLA animation at <http://tech-www.informatik.uni-hamburg.de/applets/kvd>

4

Spring 2000, Lecture 15

Field-Programmable Logic Device


- The next evolutionary step beyond the PLA is the *field-programmable logic device* (FPLD), also called the:
 - Field-programmable gate array (FPGA)
 - Complex programmable logic device (CPLD)
- FPLD characteristics
 - Based on either an array of PLA-like *and-or* structures, or on look-up tables
 - Usually includes connections from these structures to 4 nearest neighbors
 - May include long connections across chip
 - May include D (or more complex) flip-flops, to more easily build sequential circuits, possibly even RAM
 - Many can be “programmed” repeatedly
 - Available in different sizes up to 500,000 gates (100MHz, 2.5 volt, 0.25 μ , 5 metal)

5

Spring 2000, Lecture 15

Implementing a Truth Table Using a Multiplexor

 - Besides and-or structures, another alternative is to use a 4-input multiplexor




- Any function of N inputs can be implemented using a 2^N to 1 multiplexor

6

Spring 2000, Lecture 15

Implementing a Truth Table Using a Multiplexor (cont.)

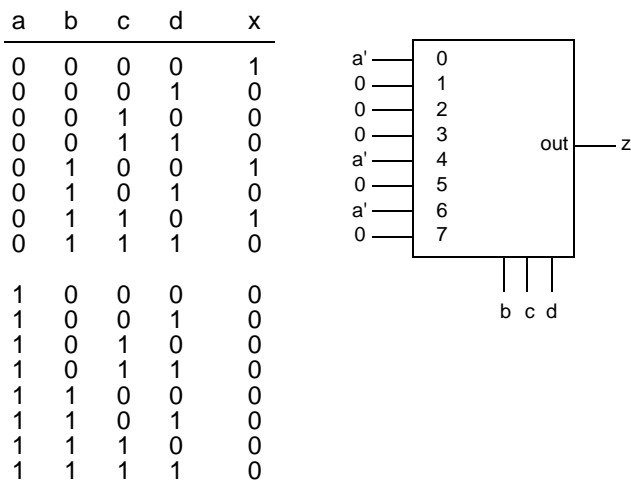- An alternative is to “fold” the truth table, and tie each input to either 1, 0, or the MSB, and only use a 3-input multiplexor




- Any function of N inputs can be implemented using a 2^{N-1} to 1 multiplexor
 - Some FPLDs are based on multiplexors, and attach simple gates to selector lines

7

Spring 2000, Lecture 15

Implementing a Truth Table Using a ROM

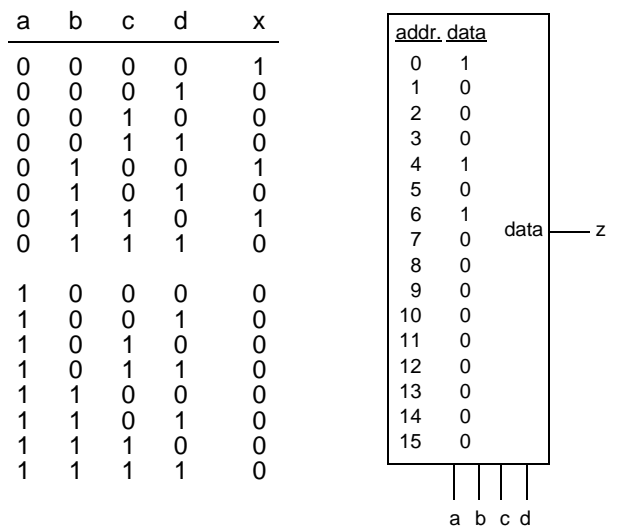- Yet another alternative is to use a ROM



- Any function of N inputs can be implemented using a $2^N \times 1$ bit ROM
 - Some FPLDs are based on static RAMs (SRAMs) loaded at power-up; these are said to use *look-up tables* (LUTs)

8

Spring 2000, Lecture 15

Different Implementation Styles

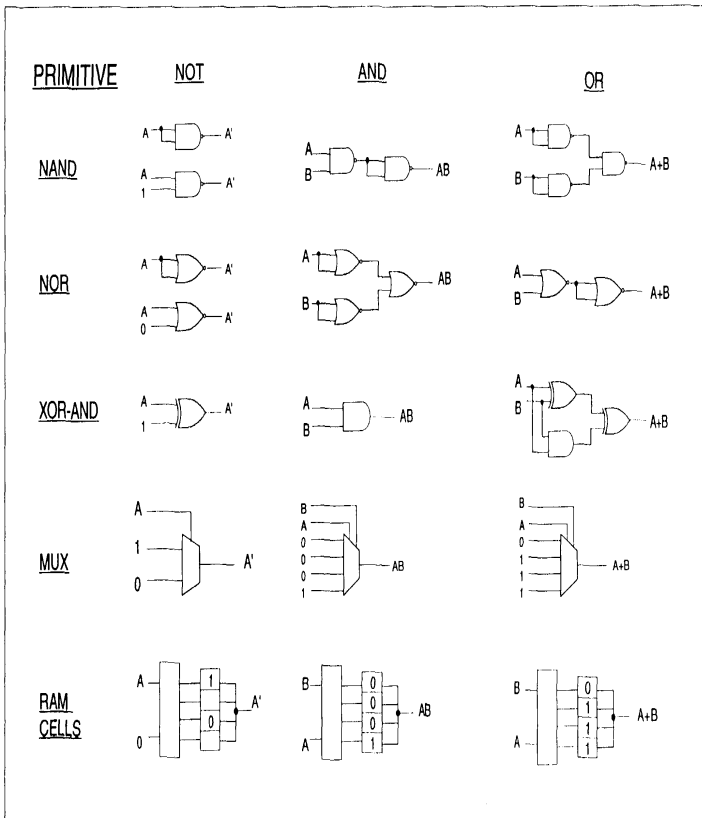


Diagram from *Digital Design Using Field Programmable Gate Arrays*,
Chan & Mourad, Prentice Hall 1994