

## Altera FLEX 8000 Block Diagram

 


Figure from Altera technical literature

- FLEX 8000 chip contains 26–162 LABs
  - Each LAB contains 8 Logic Elements (LEs), so a chip contains 208–1296 LEs, totaling 2,500–16,000 usable gates
  - LABs arranged in rows and columns, connected by FastTrack Interconnect, with I/O elements (IOEs) at the edges

1

Spring 2000, Lecture 19

## Altera FLEX 8000 Logic Array Block

 


Figure from Altera technical literature

- LAB = 8 LEs, plus local interconnect, control signals, carry & cascade chains

2

Spring 2000, Lecture 19

## Altera FLEX 8000 Logic Element

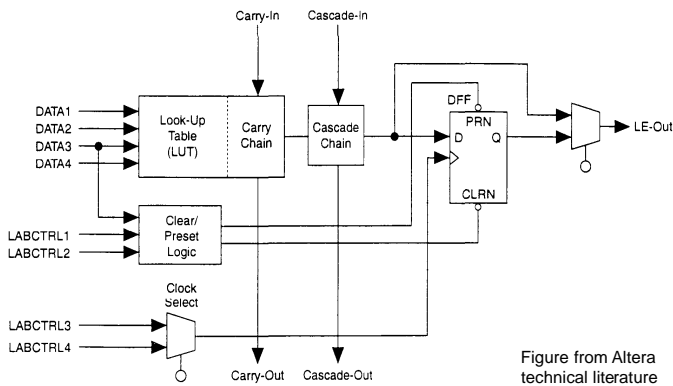


Figure from Altera technical literature

- Each Logic Element (LE) contains:
  - 4-input Look-Up Table (LUT)
    - Can produce any function of 4 variables
  - Programmable flip-flop
    - Can configure as D, T, JR, SR, or bypass
    - Has clock, clear, and preset signals that can come from dedicated inputs, I/O pins, or other LEs
  - Carry chain & cascade chain

3

Spring 2000, Lecture 19

## Altera FLEX 8000 Carry Chain (Example: n-bit adder)

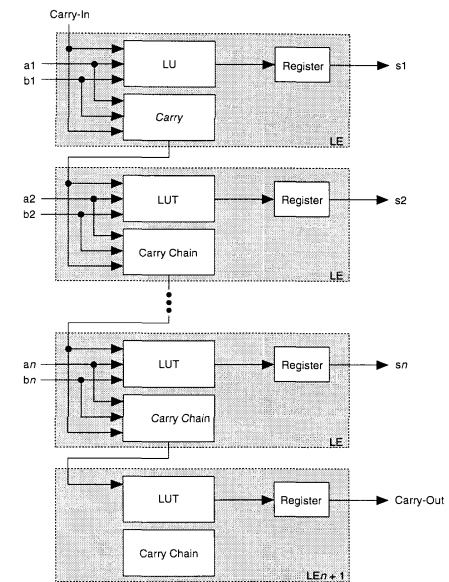


Figure from Altera technical literature

- Carry chain provides very fast (< 1ns) carry-forward between LEs
  - Feeds both LUT and next part of chain
  - Good for high-speed adders & counters

4

Spring 2000, Lecture 19

## Altera FLEX 8000 Cascade Chain


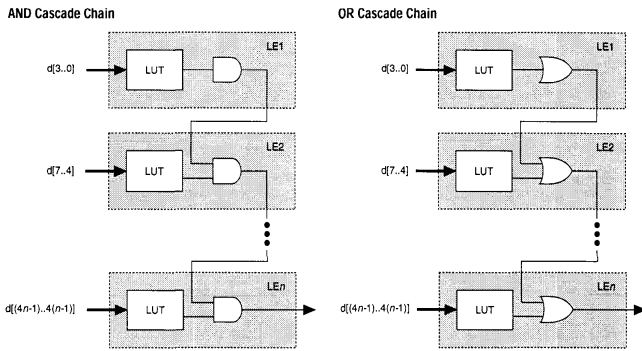


Figure from Altera technical literature


- **Cascade chain** provides wide fan-in
  - Adjacent LE's LUTs can compute parts of the function in parallel; cascade chain then serially connects intermediate values
  - Can use either a logical AND or a logical OR (using DeMorgan's theorem) to connect outputs of adjacent LEs
  - Each additional LE provides 4 more inputs to the width of the function

## Altera FLEX 8000 LE Operating Modes

### Normal

 


### Arithmetic

 

### Up/down Counter

Figure from Altera technical literature

 

- Each mode uses LE resources differently
  - 7 out of 10 inputs (4 data from LAB local interconnect, feedback from register, and carry-in & cascade-in) go to specific destinations to implement the function
  - Remaining 3 provide clock, clear, and preset for register

## Altera FLEX 8000 Operating Modes (cont.)

- **Normal mode**
  - Used for general logic applications, and wide decoding functions that can benefit from the cascade chain
- **Arithmetic mode**
  - Provides two 3-input LUTs to implement adders, accumulators, and comparators
    - One LUT provides a 3-bit function
    - Other LUT generates a carry bit
- **Up/down counter mode**
  - Provides counter enable, synchronous up / down control, and data loading options
  - Uses two 3-input LUTs
    - One LUT generates counter data
    - Other LUT generates fast carry bit
    - Use 2-to-1 multiplexer for synchronous data loading, clear and preset for asynchronous data loading

## Altera FLEX 8000 FastTrack Interconnect

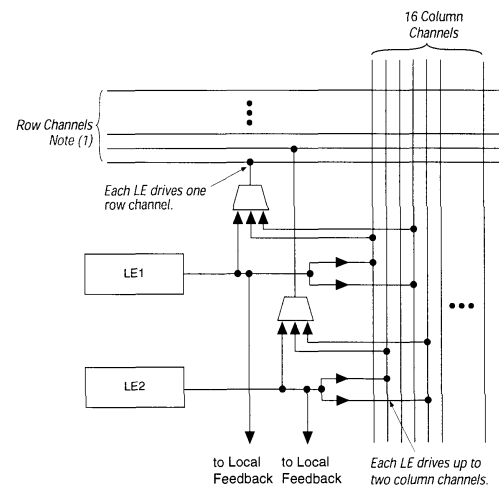


Figure from Altera technical literature

Note:  
(1) See Table 4 for the number of row channels.

- **Device-wide rows and columns**
  - Each LE in LAB drives 2 column (total 16) channels, which connects... that column
  - Each LE in LAB drives 1 row channel, which connects to other LABs in that row
    - 3-to-1 muxs connect either LE outputs or column channels to row channels

## Altera FLEX 8000 I/O Elements

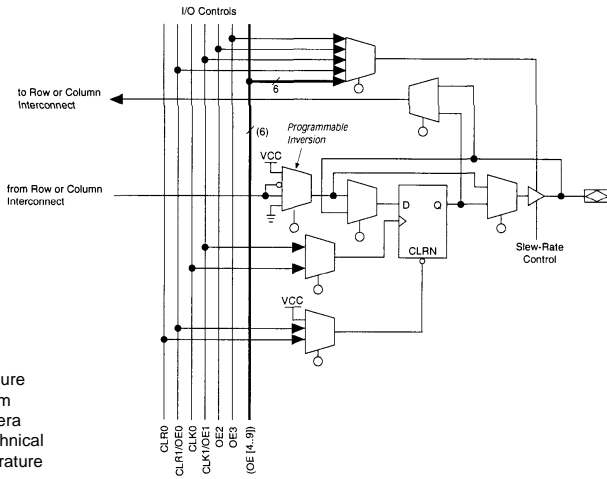


Figure from Altera technical literature

- Eight I/O Elements (IOEs) are at the end of each row and column
  - Some restrictions on how many row / column channels each IOE connects to
  - Contains a register that can be used for either input or output
    - Associated I/O pins can be used as either input, output, or bidirectional pins

## Altera FLEX 8000 Configuration

- Loading the FLEX 8000's SRAM with programming information is called *configuration*, and takes about 100ms
  - After configuration, the device initializes itself (resets its registers, enables its I/O pins, and begins normal operation)
  - Configuration & initialization = command mode, normal operation = user mode
- Six configuration schemes are available:
  - Active serial — FLEX gives configuration EPROM clock signals (not addresses), keeps getting new values in sequence
  - Active parallel up, active parallel down — FLEX 8000 gives configuration EPROM sequence of addresses to read data from
  - Passive parallel synchronous, passive parallel asynchronous, passive serial — passively receives data from some host