

Name: _____

CS 4/55111

Midterm Exam

VLSI Design

Wednesday 6 March 2002

1. Briefly distinguish between full-custom ASICs, standard-cell-based ASICs, and FPLDs, in terms of fabrication, design techniques employed, layout of components, etc. (25 points)

Name: _____

2. In studying combinational circuit design, we concentrated on the Sum-of-Products (SOP) form of Boolean expressions.

a. Why is SOP form useful and/or of particular interest? (10 points)

b. Considering the relationship between a Karnaugh map and an equivalent SOP expression, why is it desirable to make the ovals as large as possible? Be specific. (10 points)


3. Before programming a design into a FPLD, it is generally considered a good idea to verify the design's functionality using the simulator.

a. Why is simulating the design important, given it only takes a few seconds to download the design onto the FPLD where you can test the "real" design? (10 points)

Name: _____

- b. In the tutorial example with the two pushbuttons and the OR gate, why was the one pushbutton simulated with the default clock frequency, while the other was simulated with a clock frequency double the default value? (10 points)

 4. The diagram below shows how a D latch can be constructed from an SR latch.



- a. What “problem” does an SR latch have, that prompts the development of a D latch? (10 points)

- b. What is the difference between this D latch and a D flip-flop? (10 points)

Name: _____

- 5. There are many different types of FPLDs. This question explores those differences.**
- a. Between antifuse-based and SRAM-based FPLDs, which allows more chip space to be dedicated to combinational / sequential logic, and why? (10 points)**

- b. Why is it desirable to find some way to “segment” a particular track in a routing channel into two or more segments? (5 points)**