 


Implementing a Truth Table Using An And-Or Structure (Review)

- Given a truth table, we can use a Karnaugh map to find the minimum 2-level SOP implementation

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0



$$x = a'bd' + a'c'd'$$

1

Spring 2002, Lecture 10

PLAs

- A 2-level *and-or* structure is replicated many times in a programmable array called a *PLA (programmable logic array)*
 - Parts of a CPU's datapath or next-state logic can be built out of PLAs
 - Small circuits can be built out of PLAs
- At the input of each gate, there's a "fuse" which can be left whole, or broken
 - So the designer can control which inputs go to each and gate, and which outputs of the and gates go to each or gate
- A PLA can be either
 - Mask programmable — customer orders a programmed PLA from the manufacturer
 - Field programmable — customer can program PLA (once)

2

Spring 2002, Lecture 10

PLAs

- A 2-level *and-or* structure is replicated many times in a programmable array called a *PLA (programmable logic array)*

 


Diagram from *Computer Systems*, Maccabe, Irwin 1993

- This PLA has 2 inputs, 2 outputs, and can represent up to 3 product terms

3

Spring 2002, Lecture 10

PLA Example

- This is an *abstract* diagram of a PLA with 6 inputs, 4 outputs, which can represent up to 12 product terms

 


Diagram from *Digital Design*, Johnson & Karim, PWS-Kent 1987

- Try the Java KMap->PLA animation at <http://tech-www.informatik.uni-hamburg.de/applets/kvd>

4

Spring 2002, Lecture 10

Field-Programmable Logic Device

- The next evolutionary step beyond the PLA is the *field-programmable logic device* (FPLD), also called the:
 - Field-programmable gate array (FPGA)
 - Complex programmable logic device (CPLD)
- FPLD characteristics
 - Based on either an array of PLA-like *and-or* structures, or on look-up tables
 - Usually includes connections from these structures to 4 nearest neighbors
 - May include long connections across chip
 - May include D (or more complex) flip-flops, to more easily build sequential circuits, possibly even RAM
 - Many can be “programmed” repeatedly
 - Available in different sizes up to 500,000 gates (100MHz, 2.5 volt, 0.25 μ , 5 metal)

Programming Using Antifuses

- An *antifuse* is normally open (“off”); when enough current (5–15mA) passes through it it closes (“on”)
 - Current melts a thin insulating dielectric and forms a permanent silicon link
 - Disadvantage — can only program once
 - Programmed in a special hardware device
 - An antifuse FPLD may contain 750,000 antifuses, but only about 2% of them typically need to be programmed
 - Takes about 5-10 minutes for each chip
- Advantages:
 - Small — about the size of a via
 - Low resistance, low capacitance = fast
- Antifuses can be used in FPLDs to :
 - Connect inputs to cells
 - Connect cells to interconnect

Programming Using EPROMs & EEPROMs (Floating Gates)


 


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

- EPROM programming & operation:
 - To program: a high (>12V) programming voltage V_{PP} is applied to the drain, causing electrons to “jump” onto the floating gate (gate1)
 - The electrons on gate1 raise the threshold voltage V_t enough that the programmed transistor is always off
 - To erase: the transistor is exposed to UV light, which provides enough energy for the electrons stuck on gate1 to jump back onto the bulk, returning the transistor to normal operation
 - Can be reprogrammed many times

Programming Using EPROMs & EEPROMs (Floating Gates) (cont.)

- EEPROMs are similar, but are erased electrically
 - Faster to erase than EPROM, and can be done “in-circuit”
 - Requires larger cell than EPROM
- Advantages
 - Can be programmed repeatedly, in-circuit
 - Fairly small — requires only 1 transistor
- Can be used in FPLDs to :
 - Connect inputs to cells
 - In NOR gate, when transistor is programmed (disabled), an input of 1 can not pull output down to VSS
 - Connect cells to interconnect

 

Programming Using Static RAMs (SRAMs)

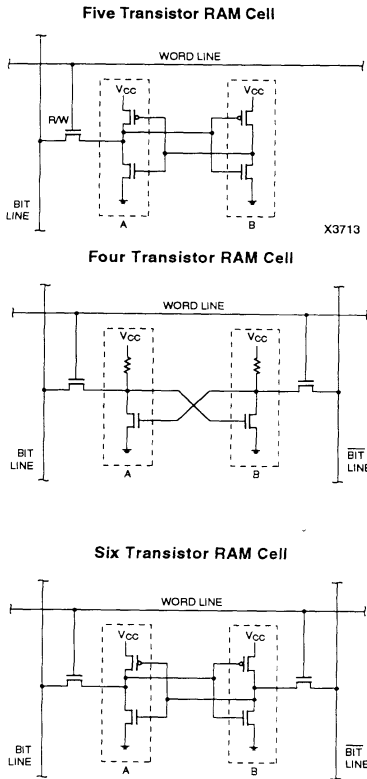


Figure from *Field-Programmable Gate Array Technology*, Trimberger, Kluwer, 1994

Programming Using Static RAMs (SRAMs) (cont.)

Disadvantages:

- Must load configuration from ROM, disk, etc. on power-up
- Large — requires several transistors

Advantages:

- Can be programmed repeatedly, in-circuit
 - Can be programmed quickly (< 1ms)
- Part has been 100% tested at factory
- Same basic process as CMOS, so quickly takes advantage of new fab processes
 - CMOS also requires less power than circuits requiring pull-up resistors

SRAMs can be used in FPLDs to :

- Connect inputs to cells, or even to replace the cell if it's a LUT
- Connect cells to interconnect

Types of FPLDs

Type of Base Cell

Programming Method	Type of Base Cell		
	Multiplexor	Look-Up Table (LUT)	AND-OR
Antifuse	Actel ACT 1, ACT 2, ACT 3 Quicklogic Crosspoint		
EPROM			Altera MAX 5000, 7000 (Salcic 2.1) Xilinx EPLD
SRAM	Plessy	Altera Flex 8000, Flex 10K (Salcic 2.2) Xilinx LCA 2000, 3000, 4000 (Salcic 2.3)	

FPGAs
CPLDs


Layout / routing

- Row-based: Actel
- Matrix-based: Altera, Quicklogic, Xilinx

Implementing a Truth Table Using a Multiplexor

Besides and-or structures, another alternative is to use a 4-input multiplexor

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

 


Any function of N inputs can be implemented using a 2^N to 1 multiplexor

Implementing a Truth Table Using a Multiplexor (cont.)

- An alternative is to “fold” the truth table, and tie each input to either 1, 0, or the MSB, and only use a 3-input multiplexor

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

 


- Any function of N inputs can be implemented using a 2^{N-1} to 1 multiplexor
 - Some FPLDs are based on multiplexors, and attach simple gates to selector lines

Implementing a Truth Table Using a ROM

- Yet another alternative is to use a ROM

a	b	c	d	x
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

 

- Any function of N inputs can be implemented using a $2^N \times 1$ bit ROM
 - Some FPLDs are based on static RAMs (SRAMs) loaded at power-up; these are said to use *look-up tables* (LUTs)

Different Implementation Styles

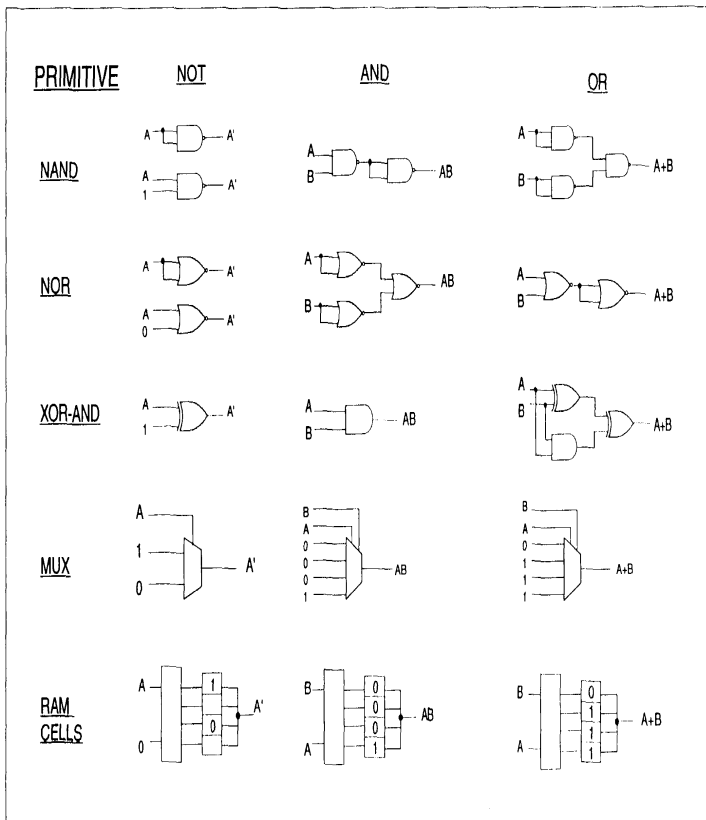


Diagram from *Digital Design Using Field Programmable Gate Arrays*, Chan & Mourad, Prentice Hall 1994