

## Types of FPLDs

### Type of Base Cell

Programming Method	Type of Base Cell		
	Multiplexor	Look-Up Table (LUT)	AND-OR
Antifuse	Actel ACT 1, ACT 2, ACT 3 Quicklogic Crosspoint		
EPROM			Altera MAX 5000, 7000 (Salcic 2.1) Xilinx EPLD
SRAM	Plessy	Altera Flex 8000, Flex 10K (Salcic 2.2) Xilinx LCA 2000, 3000, 4000 (Salcic 2.3)	

FPGAs
CPLDs

#### Layout / routing

- Row-based: Actel
- Matrix-based: Altera, Quicklogic, Xilinx

1

Spring 2002, Lecture 11

## Row-Based Layout

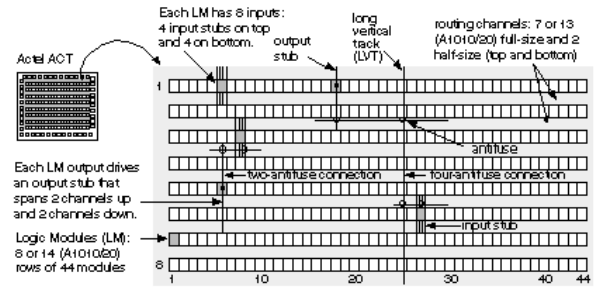


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

#### Cells are arranged in rows

- Horizontal channels between rows
- Vertical channels above cells: some short, some long
- Each *channel* contains a fixed number of *tracks*, each track holds one wire
  - Wires may be divided into fixed-length *segments* within each track
- In figure above, cell inputs connect to horizontal wires, outputs to vertical wires

2

Spring 2002, Lecture 11

## Matrix-Based Layout

 


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

#### Cells are arranged in an array (*matrix*)

- Horizontal and vertical channels between cells
- Each *channel* contains a fixed number of *tracks*, each track holds one wire
- In figure above:
  - Cell inputs connect to horizontal tracks
  - Box A connects cell output(s) to horizontal tracks, and box C connects cell output(s) to vertical tracks
  - Box B acts as a switchbox between horizontal and vertical tracks

3

Spring 2002, Lecture 11

## Antifuse Routing

 
 
 
 
 


Figure from *Field-Programmable Gate Array Technology*, Trimberger, Kluwer, 1994

4

Spring 2002, Lecture 11

## Antifuse Routing (cont.)

- Fully segmented
  - Switch at every cross point normally passes signals through vertically and horizontally, but can connect the vertical and horizontal tracks
  - Antifuse connects or disconnects the segments of the horizontal channel
- Non-segmented
  - Excessive area requirements
- 1-segment routing
  - Divides the tracks into segments of varying lengths, which allows each net to be routed in a track of more or less the appropriate size
- 2-segment routing
  - Allows track segments to be joined

5

Spring 2002, Lecture 11

## Actel ACT Routing Architecture

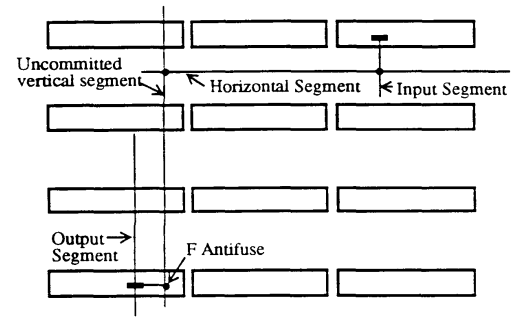


Figure 3.3.4. Routing Using Long Vertical Track (LVT)

 


Figure 3.3.5. Routing Using LVTs in another Column

Figure from *Field-Programmable Gate Array Technology*, Trimberger, Kluwer, 1994

6

Spring 2002, Lecture 11

## Actel ACT Routing Architecture (cont.)

- An Actel FPGA has rows of cells, with horizontal channels between them, and vertical “channels” called columns
- Cell inputs must come from one of the 2 adjacent horizontal tracks (either figure)
- Cell outputs can attach to:
  - A dedicated vertical track called the “output stub” (see bottom figure)
    - Output stub spans only two channels above and below the cell
  - Long vertical tracks— see top figure, where output goes to LVT instead of its dedicated output segment
    - These are vertical segments of varying lengths that can be joined together to form vertical segmented tracks

7

Spring 2002, Lecture 11

## Actel ACT Routing Architecture (cont.)

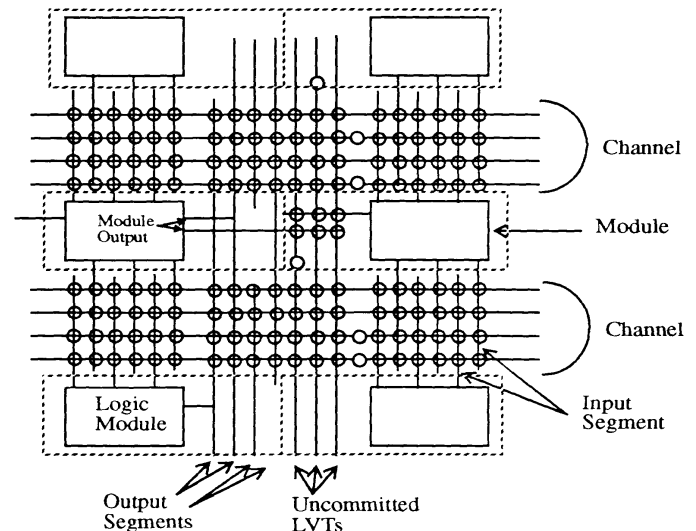


Figure from *Field-Programmable Gate Array Technology*, Trimberger, Kluwer, 1994

- Input segments connect to uncommitted horizontal segment by antifuses
  - Horizontal segments connect by antifuses
- Vertical segments pass over the cells

8

Spring 2002, Lecture 11

## Actel Act1

 


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

- Fairly simple, fine-grained logic module
  - Low delay, small area, very flexible
  - Implements basic gates, D latches, etc.
    - Can implement many functions using Shannon's Expansion Theorem
      - Any combinational function of 2 inputs
      - Almost any function of 3 inputs, many functions of 4 inputs, some functions of up to 8 inputs
- I/O modules at end of rows & columns

9

Spring 2002, Lecture 11

## Actel Act2

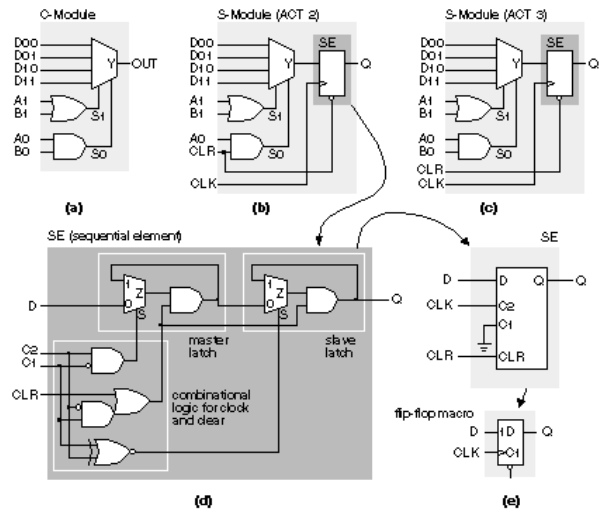


Figure from *Application-Specific Integrated Circuits*, Smith, Addison-Wesley, 1997

- C-module = combinational [sic] module
- S-module = sequential module
- Note that the timing of a particular logic macro may vary with its implementation

10

Spring 2002, Lecture 11

## Actel Act2 (cont.)

- C-module = combinational module
  - Act2 c-module provides high fan-in
    - Can implement 16 of the 20 four-input gates in the library (Act1 implements 8)
    - Implements 766 distinct combinational functions, including 13% more four-input macros and 12% more five-input macros than Act1
  - Some loss in ability to implement sequential functions
- S-module = sequential module
  - C-module plus two latches
    - Can provide rising- or falling-edge-triggered D flip-flop, or high- or low-level transparent D latch, with clear
    - Can make it look like a c-module by tying C1 to 1 and C2 to 0
    - Need two or more s-modules to build J-K or more complex flip-flops

11

Spring 2002, Lecture 11