

## Summary

### Flip flops v. latches

- Flip flops are edge triggered
- Latches are level sensitive

### Many variants

- S-R, J-K, D, T latch/flip-flop
- D-type most useful in processor design

### Beware of race conditions

- Need edge triggered device in any feed-back path


## State machines design

Interesting state machines have inputs and outputs.


State will change depending on input.

Two classes are Mealy and Moore:

 - Moore machine:  $\text{output} = f(\text{state})$



 Mealy machine:  $\text{output} = f(\text{state}, \text{input})$



Generally: Moore machines have more states (mnemonic), but are easier to understand.

## Design Process

### General Procedure

- Step 1: Create a State Diagram
- Step 2: Write down a State Transition Table
- Step 3: Figure out the inputs to the flip flops using the excitation table.
- Step 4: Figure out functions for input to flip flops
- Step 5: Implement the machine

### Example

- "Write a string recognizer that recognizes the pattern 010 in its input.
- When an input bit pattern is recognized, output a 1.
- When the sequence 100 is seen, output zeros thereafter until a reset is asserted"
- Examples:

X: 001010100010

Z: 000101010000


X: 0110110100100

Z: 0000000010000


## 1. State diagram creation

Start with easy paths, fill in the rest, reuse as much as possible!

This is a **Moore** machine:

 

2. Final state diagram

 


3. Symbolic State Transition Table:

| State Number | Current State | Next (X=0) | Next (X=1) | Output |
|--------------|---------------|------------|------------|--------|
|              | S0            |            |            |        |
|              | S1            |            |            |        |
|              | S2            |            |            |        |
|              | S3            |            |            |        |
|              | S4            |            |            |        |
|              | S5            |            |            |        |
|              | S6            |            |            |        |

4. Figure out flip flop inputs

|          |          |          |          |           |           |           |
|----------|----------|----------|----------|-----------|-----------|-----------|
| <b>A</b> | <b>B</b> | <b>C</b> | <b>X</b> | <b>A'</b> | <b>B'</b> | <b>C'</b> |
| 0        | 0        | 0        | 0        |           |           |           |
| 0        | 0        | 0        | 1        |           |           |           |
| 0        | 0        | 1        | 0        |           |           |           |
| 0        | 0        | 1        | 1        |           |           |           |
| 0        | 1        | 0        | 0        |           |           |           |
| 0        | 1        | 0        | 1        |           |           |           |
| 0        | 1        | 1        | 0        |           |           |           |
| 0        | 1        | 1        | 1        |           |           |           |
| 1        | 0        | 0        | 0        |           |           |           |
| 1        | 0        | 0        | 1        |           |           |           |
| 1        | 0        | 1        | 0        |           |           |           |
| 1        | 0        | 1        | 1        |           |           |           |
| 1        | 1        | 0        | 0        |           |           |           |
| 1        | 1        | 0        | 1        |           |           |           |
| 1        | 1        | 1        | 0        |           |           |           |
| 1        | 1        | 1        | 1        |           |           |           |

5. Reduce using K-maps

 

### 6. Output Logic

A B C Output


|   |   |   |   |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | X |

Karnaugh map

|   |    |    |    |    |    |
|---|----|----|----|----|----|
|   | AB | 00 | 01 | 11 | 10 |
| C | 0  | 0  | 2  | 6  | 4  |
|   | 1  | 1  | 3  | 7  | 5  |

O =

### 6. Final Circuit

 

### State minimization

**Goal:** to minimize the number of states in a state diagram.

- Basic idea: Identify and combine states with equivalent behavior.
- 2 states are equivalent if the output is the same and, for each input combinations, the next state is the same state or an equivalent state.

**Approach:**

- Start with state transition table.
- Identify states with the same behavior
- If such states go to the same next state, combine them and rename each occurrence of the old state in the state table.
- Repeat with new state table until no new combinations are possible.

Next Time : Minimization

### State Transition Table

| Prefix | Name | X=0 | X=1 | Output (X=0) | Output (X=1) |
|--------|------|-----|-----|--------------|--------------|
| Reset  | S0   | S1  | S2  | 0            | 0            |
| 0      | S1   | S3  | S4  | 0            | 0            |
| 1      | S2   | S5  | S6  | 0            | 0            |
| 00     | S3   | S7  | S8  | 0            | 0            |
| 01     | S4   | S9  | S10 | 0            | 0            |
| 10     | S5   | S11 | S12 | 0            | 0            |
| 11     | S6   | S13 | S14 | 0            | 0            |
| 000    | S7   | S0  | S0  | 0            | 0            |
| 001    | S8   | S0  | S0  | 0            | 0            |
| 010    | S9   | S0  | S0  | 0            | 0            |
| 011    | S10  | S0  | S0  | 1            | 0            |
| 100    | S11  | S0  | S0  | 0            | 0            |
| 101    | S12  | S0  | S0  | 1            | 0            |
| 110    | S13  | S0  | S0  | 0            | 0            |
| 111    | S14  | S0  | S0  | 0            | 0            |


## Modified State Transition Table

| Prefix                    | Name | X=0 | X=1  | Output (X=0) | Output (X=1) |
|---------------------------|------|-----|------|--------------|--------------|
| Reset                     | S0   | S1  | S2   | 0            | 0            |
| 0                         | S1   | S3  | S4   | 0            | 0            |
| 1                         | S2   | S5  | S6   | 0            | 0            |
| 00                        | S3   | S7' | S7'  | 0            | 0            |
| 01                        | S4   | S7' | S10' | 0            | 0            |
| 10                        | S5   | S7' | S10' | 0            | 0            |
| 11                        | S6   | S7' | S7'  | 0            | 0            |
| 00x,<br>010<br>100<br>11x | S7'  | S0  | S0   | 0            | 0            |
| 011<br>101                | S10' | S0  | S0   | 1            | 0            |

## Modified State Transition Table (2nd iteration)

| Prefix                    | Name | X=0 | X=1  | Output (X=0) | Output (X=1) |
|---------------------------|------|-----|------|--------------|--------------|
| Reset                     | S0   | S1  | S2   | 0            | 0            |
| 0                         | S1   | S3' | S4'  | 0            | 0            |
| 1                         | S2   | S4' | S3'  | 0            | 0            |
| 11                        | S3'  | S7' | S7'  | 0            | 0            |
| 01, 10                    | S4'  | S7' | S10' | 0            | 0            |
| 00x,<br>010<br>100<br>11x | S7'  | S0  | S0   | 0            | 0            |
| 011<br>101                | S10' | S0  | S0   | 1            | 0            |

## State Diagram:

 

## Summary

### Components

- Flip flops (edge triggered)
- Latches (usually level triggered).

### Designing Sequential Circuits

- Step 1: Create a State Diagram
- Step 2: Write down a State Transition Table
- Step 3: Do state minimization
- Step 4: Do state assignment
- Step 5: Figure out the inputs to the flip flops using the excitation table.
- Step 6: Figure out functions for input to flip flops