

Introduction to Design Using AHDL

Kevin Schaffer
Kent State University
Spring 2006

HDLs

- For large designs, hardware description languages (HDLs) are usually better than schematic capture
- Permits both behavioral and structural description of logic
- HDLs are concurrent, programming languages are sequential!

2

AHDL

- Altera Hardware Description Language
- Proprietary HDL for use with Altera's field-programmable logic devices and tools
- Simple syntax, easy to learn
- AHDL files have a TDF extension

3

Subdesign Section

- Declares component's name
 - Component name and file name must match
- Declares ports
 - Name
 - Input, output, or bidirectional
 - Width (if it is a group)
- Required

4

Logic Section

- Defines the logical operation of the component
- Last section in the TDF file
- Required


5

Combinational Logic (TDF)

```
SUBDESIGN bool1
(
  a0, a1, b0, b1: INPUT;
  s0, s1: OUTPUT;
)
BEGIN
  s0 = a0 & a1 & !b1;
  s1 = s0 # b0;
END;
```

6

Combinational Logic (GDF)

 

7

AHDL Syntax

- Identifiers and keywords are case-insensitive (unlike C/C++)
- Whitespace is not significant
- Statements end with a semicolon (;)
- Put comments between percent signs (%)

8

Boolean Expressions

- Operators
 - AND (&)
 - OR (#)
 - NOT (!)
- Constants
 - VCC
 - GND

9

Variables Section

- Declares internal named nodes
- Declares instances of primitives and macrofunctions
- Must follow subdesign section
- Optional


10

Named Node (TDF)

```
SUBDESIGN bool2
(
  a0, a1, b0, b1: INPUT;
  s1: OUTPUT;
)
VARIABLE
  inter: NODE;
BEGIN
  inter = a0 & a1 & !b1;
  s1 = inter # b0;
END;
```

11

Named Node (GDF)

 

12

Groups

- Multiple bits treated as a single unit
- Range of indexes goes after the group name enclosed in square brackets
 - `a[15..0]`
- Use `[]` as shorthand for the entire group
- Interpreted as unsigned binary numbers in arithmetic operations

13

Group Operations

- Assignment
 - `a[15..8] = b[7..0];`
 - `a[] = b[];`
- Assignment from a single node
 - `a[4..0] = inter;`
 - `a[] = VCC;`
- Arithmetic
 - `c[15..0] = a[15..0] + b[15..0];`

14

Address Decoder

```
SUBDESIGN decode
(
  address[15..0]: INPUT;
  chip_enable1, chip_enable2: OUTPUT;
)
BEGIN
  chip_enable1 = (address[15..0] == H"FF30");
  chip_enable2 = (address[15..0] == H"FF50");
END;
```

15

Constants

- Literals
 - Decimal: `65328`
 - Hexadecimal: `H"FF30"`
 - Binary: `B"1111111100110000"`
- Can be assigned to groups or used with group arithmetic operators
- Use **CONSTANT** statement to declare named constants

16

Named Constants

```
CONSTANT IO_ADDRESS1 = H"FF30";
CONSTANT IO_ADDRESS2 = H"FF50";

SUBDESIGN decode
(
  address[15..0]: INPUT;
  chip_enable1, chip_enable2: OUTPUT;
)
BEGIN
  chip_enable1 = (address[] == IO_ADDRESS1);
  chip_enable2 = (address[] == IO_ADDRESS2);
END;
```

17

Conditional Logic

- **IF** statement
 - Select operation based on a set of Boolean expressions
 - Similar to `if` in C/C++
- **CASE** statement
 - Select operation based on the value of a group/node
 - Similar to `switch` in C/C++

18

Multiplexor

```
SUBDESIGN mux
(
  a, b, sel: INPUT;
  result: OUTPUT;
)
BEGIN
  IF sel == 0 THEN
    result = a;
  ELSE
    result = b;
  END IF;
END;
```

19

Priority Encoder (1)

```
SUBDESIGN priority
(
  prior4: INPUT;
  prior3: INPUT;
  prior2: INPUT;
  prior1: INPUT;
  prior_code[2..0]:
    OUTPUT;
)
```

prior				prior_code
4	3	2	1	(decimal)
1	x	x	x	4
0	1	x	x	3
0	0	1	x	2
0	0	0	1	1
0	0	0	0	0

20

Priority Encoder (2)

```
IF prior4 THEN
    prior_code[] = 4;
ELSIF prior3 THEN
    prior_code[] = 3;
ELSIF prior2 THEN
    prior_code[] = 2;
ELSIF prior1 THEN
    prior_code[] = 1;
ELSE
    prior_code[] = 0;
END IF;
```

21

Binary to One-Hot Decoder

```
SUBDESIGN decoder_2_to_4
( inpcod[1..0]: INPUT;
  outcod[3..0]: OUTPUT; )
BEGIN
    CASE inpcod[] IS
        WHEN 0 => outcod[] = B"0001";
        WHEN 1 => outcod[] = B"0010";
        WHEN 2 => outcod[] = B"0100";
        WHEN 3 => outcod[] = B"1000";
    END CASE;
END;
```

22

Truth Tables

- Map arbitrary input patterns to outputs
- First line declares which inputs and outputs the table maps
- Subsequent lines define the input patterns and corresponding outputs
- Input patterns can contain "don't cares" (x)

23

Decoder with Truth Table

```
SUBDESIGN decoder
( inp[1..0]: INPUT;
  a, b, c, d: OUTPUT; )
BEGIN
    TABLE
        inp[1..0] => a, b, c, d;
        H"0"      => 1, 0, 0, 0;
        H"1"      => 0, 1, 0, 0;
        H"2"      => 0, 0, 1, 0;
        H"3"      => 0, 0, 0, 1;
    END TABLE;
END;
```

24

Advanced Address Decoder

```
SUBDESIGN decode2
( addr[15..0], m/io: INPUT;
  rom, ram, print, inp[2..1]: OUTPUT; )
BEGIN
  TABLE
    m/io, addr[15..0] => rom, ram, print, inp[];
    1, B"00xxxxxxxxxxxxxxxx" => 1, 0, 0, B"00";
    1, B"10xxxxxxxxxxxxxxxx" => 0, 1, 0, B"00";
    0, B"0000001010000000" => 0, 0, 0, B"00";
    0, B"0000110100010000" => 0, 0, 0, B"01";
  END TABLE;
END;
```

25

Primitives & Macrofunctions

- Primitives are built-in components
 - Examples: **TRI**, **DFE**
- Macrofunctions are user-defined components
- Can be instantiated in the variables section or inline in a Boolean expression (like a function)
- Macrofunctions must be declared, typically using an include file

26

Instantiating Macrofunctions

- Declare the macrofunction instance in the variables section
 - **ff: DFE;**
- Connect the ports in the logic section
 - **ff.d = data_in;**
 - **data_out = ff.q;**

27

1-bit Register

```
SUBDESIGN reg1
(
  clk, load, d: INPUT; q: OUTPUT;
)
VARIABLE
  ff: DFE;
BEGIN
  ff.clk = clk;
  ff.ena = load;
  ff.d = d;
  q = ff.q;
END;
```

28

Inline Macrofunctions

- You can instantiate and connect a macrofunction within an expression
 - `data_out = DFF(data_in, clk, ,);`
- Unused inputs can be left out, but the commas are required

29

1-bit Register (Inline)

```
SUBDESIGN reg1b
(
  clk, load, d: INPUT;
  q: OUTPUT;
)
BEGIN
  q = DFFE(d, clk, , , load);
END;
```

30

Groups of Macrofunctions

- You can instantiate a group of macrofunctions just like a group of nodes
 - `ff[7..0]: DFFE;`
- Then connect all the ports of a group at once
 - `ff[7..0].clk = clk;`
 - `ff[7..0].d = data_in[7..0];`
- Pay attention to where the []'s go


31

8-bit Register (TDF)

```
SUBDESIGN register
(
  clk, load, d[7..0]: INPUT; q[7..0]: OUTPUT;
)
VARIABLE
  ff[7..0]: DFFE;
BEGIN
  ff[].clk = clk;
  ff[].ena = load;
  ff[].d = d[];
  q[] = ff[].q;
END;
```

32

8-bit Register (GDF)

 

33

Bidirectional Ports

- Can be used as both inputs and outputs
- Driven by a tristate buffer (**TRI**)
 - Tristate buffer has an output enable input
 - When output enable is low, buffer goes into a high-impedance state
- Internal nodes cannot be bidirectional

34


Bus Register (TDF)

```

SUBDESIGN bus_reg
(
  clk, oe: INPUT;
  io: BIDIR;
)
BEGIN
  io = TRI(DFP(io, clk, , ), oe);
END;
    
```

35

Bus Register (GDF)

 

36

Declaring Macrofunctions

- Macrofunctions (but not primitives) must be declared before use
 - `FUNCTION bus_reg(clk, oe) RETURNS (io);`
- Typically the declaration is placed in an include (.inc) file and then **INCLUDE**'d in a TDF

37

4-bit Bidirectional Port

```
FUNCTION bus_reg(clk, oe) RETURNS (io);

SUBDESIGN bidir
(
  clk, oe: INPUT; io[3..0]: OUTPUT;
)
BEGIN
  io0 = bus_reg(clk, oe);
  io1 = bus_reg(clk, oe);
  io2 = bus_reg(clk, oe);
  io3 = bus_reg(clk, oe);
END;
```

38

Registered Outputs

```
SUBDESIGN reg_out
(
  clk, load, d[7..0]: INPUT;
  q[7..0]: OUTPUT;
)
VARIABLE
  q[7..0]: DFFE;
BEGIN
  q[].clk = clk;
  q[].ena = load;
  q[] = d[];
END;
```

39

16-bit Loadable Counter (1)

```
SUBDESIGN loadable_counter
(
  clock, load, enable, reset: INPUT;
  d[15..0]: INPUT;
  q[15..0]: OUTPUT;
)
VARIABLE
  count[15..0]: DFFE;
```

40

16-bit Loadable Counter (2)


```
count[].clk = clock;
count[].clrn = !reset;

IF load THEN
  count[].d = d[];
ELSIF enable THEN
  count[].d = count[].q + 1;
ELSE
  count[].d = count[].q;
END IF;

q[] = count[].q;
```


41

State Machines

 

42

Flip-Flop as a State Machine

 

43

Flip-Flop State Machine (1)

```
SUBDESIGN d_flip_flop
(
  clock, reset, d: INPUT;
  q: OUTPUT;
)
VARIABLE
  ss: MACHINE WITH STATES (s0, s1);
BEGIN
  ss.clk = clock;
  ss.reset = reset;
```

44

Flip-Flop State Machine (2)

```
CASE ss IS
  WHEN s0 =>
    q = GND;
    IF d THEN
      ss = s1;
    END IF;
  WHEN s1 =>
    q = VCC;
    IF !d THEN
      ss = s0;
    END IF;
END CASE;
```

45

Flip-Flop State Machine (3)

```
CASE ss IS
  WHEN s0 =>
    IF d THEN ss = s1; END IF;
  WHEN s1 =>
    IF !d THEN ss = s0; END IF;
END CASE;

CASE ss IS
  WHEN s0 => q = GND;
  WHEN s1 => q = VCC;
END CASE;
```

46

State Machine Ports

- Clock (**clk**)
 - Required
- Asynchronous Reset (**reset**)
 - Active-High
- Clock Enable (**ena**)

47

Moore Machine (1)

```
SUBDESIGN manual_state_assignment
(
  clock, reset, ccw, cw: INPUT;
  phase[3..0]: OUTPUT;
)
VARIABLE
  ss: MACHINE OF BITS (phase[3..0])
  WITH STATES (s0 = B"0001",
              s1 = B"0010",
              s2 = B"0100",
              s3 = B"1000");
```

48

Moore Machine (2)

```
TABLE
  ss, ccw, cw => ss;

  s0, 1, x => s3;
  s0, x, 1 => s1;
  s1, 1, x => s0;
  s1, x, 1 => s2;
  s2, 1, x => s1;
  s2, x, 1 => s3;
  s3, 1, x => s2;
  s3, x, 1 => s0;
END TABLE;
```

49

Mealy Machine (1)

```
SUBDESIGN mealy
(
  clock, reset, y: INPUT;
  z: OUTPUT;
)
VARIABLE
  ss: MACHINE WITH STATES (s0, s1, s2, s3);
```

50

Mealy Machine (2)

```
TABLE
  ss, y => z, ss;

  s0, 0 => 0, s0;
  s0, 1 => 1, s1;
  s1, 0 => 0, s1;
  s1, 1 => 1, s2;
  s2, 0 => 0, s2;
  s2, 1 => 1, s3;
  s3, 0 => 0, s3;
  s3, 1 => 1, s0;
END TABLE;
```

51