

## Topic 9: Building Blocks for Computers

Readings for this topic:

P&H, Appendix B.3 thru B.6

### Goal


- Summary of combinatorial and sequential components that are useful for computers.
- Techniques for combining them

## Recall: Full Adder

### Boolean Algebra

$$Sum = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$C_{out} = AB + BC + AC$$

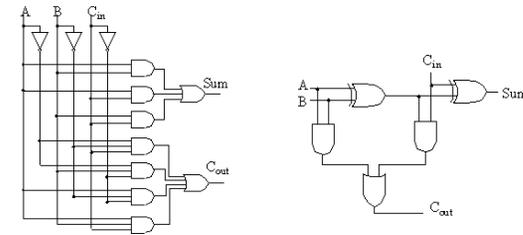


## Bit Slice Adders

### Problem: How to add 3 bit numbers?

- $C_2C_1C_0 = A_2A_1A_0 + B_2B_1B_0$
- Redesigning circuit for 6 inputs would be messy and wouldn't scale well.

Solution: Cascade 1-bit adders


A	B	C <sub>in</sub>	Sum	Cont
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

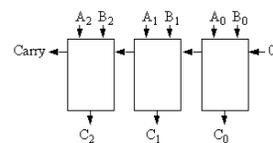

## Adder bit slice
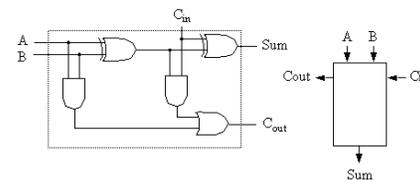
### This is called a "full adder".


- A "half adder" adds *two* bits and produces sum and carry out



## Bit-slice Adder

Problem: Time to compute carry grows with number of inputs


Solution: Carry look ahead adders.

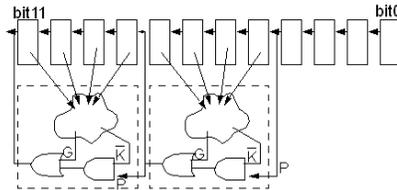

- shortcut the carry from previous group of bits to following group of bits
- How: using *local* group of bits, determine:
  - generate: group will always generate carry into next group
  - kill: group will never generate carry into next group
  - propagate: group will propagate carry from previous group into next

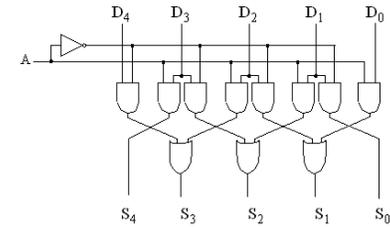
## Shifters

Shifts 1 bit left/right, based on input: 1 => shift left, 0 => shift right


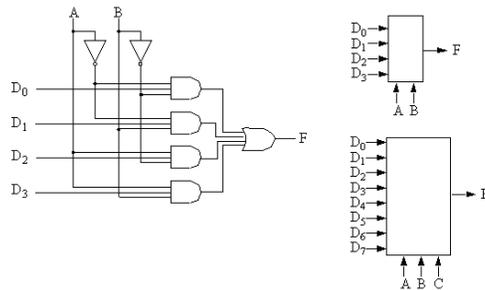
## Multiplexer

Given an n-bit number as input, select one of  $2^n$  inputs.




AND gate passes signal through if the control is 1

## Full Shifter

Shift N-bit number N positions in one direction

Can build a shifter with multiplexors

Example: 4-bit right-shifter

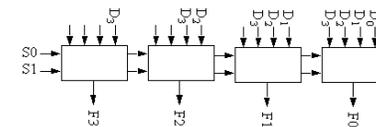

**Example: to make full 32-bit shifter, use 3 stages:**

- stage1: shift by 0, 8, 16, or 24
- stage2: shift by 0, 2, 4, or 6
- stage3: shift by 0, or 1

# ALU

**Summary: we can do shifters, adders, AND, OR, NOT, XOR, ...**

- Arithmetic operations generate a carry
- Logic operations have no carry


**An ALU computes a function of 2 inputs  $O = F(A, B)$ , where the function  $F$  is selected by other inputs ( $F_0, F_1$ ).**

- Bit Slicing: Compute function for 1 bit using carry in and carry out. This is just a generalization of cascaded adders.

# An example ALU

F	Function
00	A AND B
01	A OR B
10	NOT B
11	A + B


# Circuit Symbol

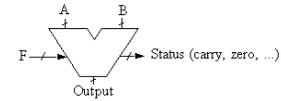


# Decoders

**How do we select an operation?**

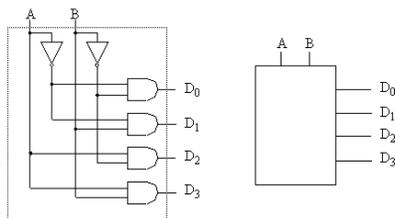**Decoder: given an n-bit number as input, enables one of 2n outputs**



# ALU Bit Slice Schematic

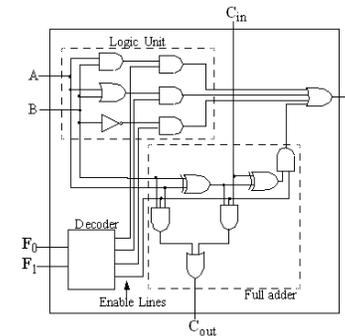

# ALU Schematic

