

Subtraction

Add: input A and B, Cin=0

Subtract: input A and B, Cin=1


How come? remember two's complement...

Building Registers

Abstraction:

- Inputs: data[N], clock, write-enable
- Output: data[N]

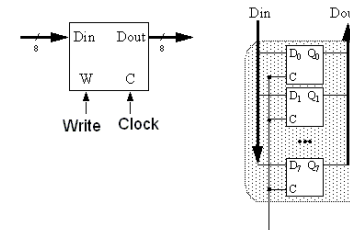Using D Flip-flops, we almost get it (e.g., 8 bit register):




Problem: How do we do write-enable?

N-bit Registers

Implementing write-enable


Solution 1: Gate clock.

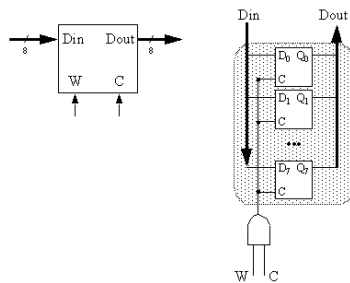

What are the problems with this solution?

N-bit Registers

Solution 2: Use multiplexor (MUX):

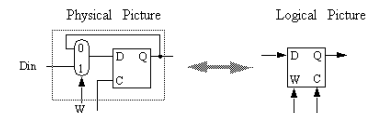


By connecting together N of the writable D Flip-flops, N bit register can be implemented.


N-bit Register

Solution 3: Use special FF that have enable "built-in"

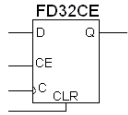- Xilinx FD32CE (Flip-flop, Data input, Clear input, clock Enable):



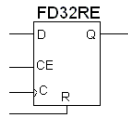Xilinx FD32RE (Flip-flop, Data input, Reset input, clock Enable)




Remember: never gate clocks!

Register Files

Abstraction

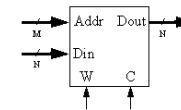- holds $2M$ (e.g., $M=4$, $24=16$) registers.
- Inputs: Register Number $[M]$, Din $[N]$, Clock, Write-enable
- Outputs: Dout $[N]$




Example:

- Addr=0011, W=0
Dout = Reg[3]
- Addr=0101, W=1, Din=0xFF
Reg[5] = 0xFF at clock

Register File with mux

How to select a register

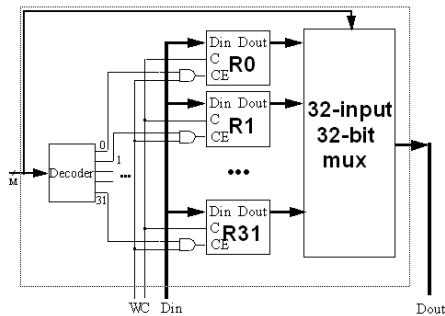


Tri-state outputs

Normal outputs can be 0 or 1


Tri-state outputs can also be *off* ("disabled", on: "enabled")

This allows many outputs to be wired together

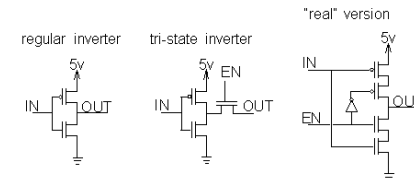- as long as only *one* is enabled at a time!




Register File with tri-state

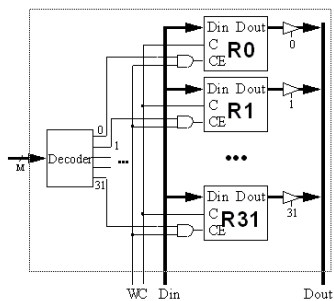

Hint: For HOT314 we will implement the register file using a RAM.


What goes in a RAM?

Example: 128 x 1-bit memory ($128=8*16$)

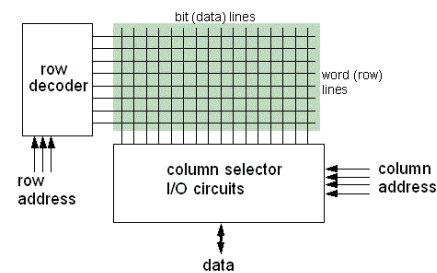

SRAM Cells

6-T static RAM cell

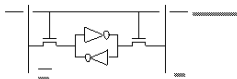

Read:


- pull bit + bit to V_{cc}
- pull 1 row select high
- cell pulls bit or bit low
- sense amp detects differential signal between bit and bit

Write:

- pull 1 row select high
- drive bit and bit to flip cell

DRAM Cells

1-T dynamic RAM cell

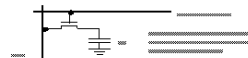

Read:

- pull bit $V_{cc}/2$
- pull 1 row select high
- cell "nudges" bit low or high
- sense amp detects difference to a reference bit line

Write:

- pull 1 row select high
- drive bit line to charge/discharge capacitor