

VHDL Introduction, Part I

Figures in this lecture are from:

*Rapid Prototyping of Digital Systems,
Second Edition*
James O. Hamblen & Michael D. Furman,
Kluwer Academic Publishers, 2001,
ISBN 0-7923-7439-8

Dr. Robert A. Walker

Computer Science Department
Kent State University
Kent, OH 44242 USA

<http://www.cs.kent.edu/~walker>

VHDL History

- **VHDL = VHSIC Hardware Description Language**
 - VHSIC = Very High Speed Integrated Circuits
 - Both US Department of Defense (DOD) programs
- **Initially developed under DOD auspices, later standardized as IEEE standards 1076-1987, 1076-1993, & 1076-1164 (standard logic data type)**
- **Syntax similar to ADA and Pascal**
- **A concurrent language, initially aimed at simulation, later at synthesis**
 - Specific subsets and “cookbook” design styles supported by logic and behavioral synthesis tools
 - Write code like this & you’ll get this expected design...


Signals, Time, and Simulation

- **Variables vs. signals**
 - VHDL *variables* change value without delay
 - VHDL *signals* have an associated delay
- **A signal is given a value at a specific point in time, and retains that value until it is given a new value**
 - A *waveform* is a sequence of values over time
 - Example: in1 <= '0', '1' after 5 ns, '0' after 15 ns;
 - A variable has a single value, whereas a signal has multiple value / time pairs
- **A discrete event simulator executes VHDL code by advancing time to the next event, updating signal values, then possibly scheduling new events**

3

Spring 2006, Lecture 18

Simple Gate Network (Desired Hardware)

 

4

Spring 2006, Lecture 18

Simple Gate Network (VHDL Code)

```

LIBRARY IEEE;                                -- Include Libraries for standard logic data types
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY gate_network IS                        -- Entity name normally the same as file name
    PORT (A, B, C : IN STD_LOGIC;          -- Ports: Declares module inputs and outputs
          D       : IN STD_LOGIC_VECTOR(3 DOWNTO 0); -- Standard Logic Vector ( Array of 4 Bits )
          X, Y    : OUT STD_LOGIC );       -- Output Signals

END gate_network;

-- Defines internal module architecture
ARCHITECTURE behavior OF gate_network IS
BEGIN                                       -- Concurrent assignment statements operate in parallel
    X <= A AND NOT( B OR C ) AND ( D( 1 ) XOR D( 2 ) );
    -- D(1) selects bit 1 of standard logic vector D
    -- Process must declare a sensitivity list,
    -- In this case it is ( A, B, C, D )
    -- List includes all signals that can change the outputs

    PROCESS ( A, B, C, D )
    BEGIN                                   -- Statements inside process execute sequentially
        Y <= A AND NOT( B OR C ) AND ( D( 1 ) XOR D( 2 ) );
    END PROCESS;
END behavior;

```

5

Spring 2006, Lecture 18

VHDL Design Styles

- **VHDL was designed to support both behavioral and structural designs as various levels of abstraction**
 - *Behavioral description* says what the design does, but not how it is implemented
 - *Structural description* specifies the interconnection of a set of components, but not what the components do
 - The design process tends to convert high-level behavioral descriptions to low-level structural ones
- **VHDL design entities include**
 - *Entity* declaration — interface (named I/O ports)
 - *Architecture* declaration — behavioral or structural description of the design entity

6

Spring 2006, Lecture 18


Simple Gate Network (Entity)

```

LIBRARY IEEE;                                -- Include Libraries for standard logic data types
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY gate_network IS                        -- Entity name normally the same as file name
  PORT (A, B, C : IN STD_LOGIC;             -- Ports: Declares module inputs and outputs
        D       : IN STD_LOGIC_VECTOR(3 DOWNTO 0); -- Standard Logic Vector ( Array of 4 Bits )
        X, Y    : OUT STD_LOGIC );         -- Output Signals
END gate_network;

```

 

7

Spring 2006, Lecture 18


Simple Gate Network (Architecture)

```

-- Defines internal module architecture
ARCHITECTURE behavior OF gate_network IS
  BEGIN
    -- Concurrent assignment statements operate in parallel
    -- D(1) selects bit 1 of standard logic vector D
    X <= A AND NOT( B OR C ) AND ( D( 1 ) XOR D( 2 ) );
    -- Process must declare a sensitivity list,
    -- In this case it is ( A, B, C, D )
    -- List includes all signals that can change the outputs

    PROCESS ( A, B, C, D )
      BEGIN
        -- Statements inside process execute sequentially
        Y <= A AND NOT( B OR C ) AND ( D( 1 ) XOR D( 2 ) );
      END PROCESS;
  END behavior;

```

 

8

Spring 2006, Lecture 18

VHDL Data Types

- Boolean, integer, real
- STD_LOGIC to model logic values
 - 0, 1, Z, U, X, -, L, W, H
 - Z = tri-state, U = uninitialized, X = unknown, - = don't care, L = weak "0", W = weak unknown, H = weak "1"

Table 6.2 STD_LOGIC conversion functions.

Function	Example:
TO_STDLOGICVECTOR (<i>bit_vector</i>) Converts a bit vector to a standard logic vector.	TO_STDLOGICVECTOR (X"FFFF") Generates a 16-bit standard logic vector of ones. "X" indicates hexadecimal and "B" is binary.
CONV_STD_LOGIC_VECTOR (<i>integer, bits</i>) Converts an integer to a standard logic vector.	CONV_STD_LOGIC_VECTOR (7, 4) Produces a standard logic vector of "0111".
CONV_INTEGER (<i>std_logic_vector</i>) Converts a standard logic vector to an integer.	CONV_INTEGER ("0111") Produces an integer value of 7.

VHDL Operations

Precedence:

- ** , ABS, NOT
- *, /, MOD, REM
- + , - (sign)
- + , - , &
- SLL, SRL, SLA, ...
- =, / =, <, < =, >, > =
- AND, NOT, OR, NOT, XOR, XNOR
- (note: all at same level)

Table 6.1 VHDL Operators.

VHDL Operator	Operation
+	Addition
-	Subtraction
*	Multiplication*
/	Division*
MOD	Modulus*
REM	Remainder*
&	Concatenation ‡ used to combine bits
SLL**	logical shift left
SRL**	logical shift right
SLA**	arithmetic shift left
SRA**	arithmetic shift right
ROL**	rotate left
ROR**	rotate right
=	equality
/=	Inequality
<	less than
<=	less than or equal
>	greater than
>=	greater than or equal
NOT	logical NOT
AND	logical AND
OR	logical OR
NAND	logical NAND
NOR	logical NOR
XOR	logical XOR
XNOR*	logical XNOR

*Not supported in many VHDL synthesis tools. In the MAX+PLUS II tools, only multiply and divide by powers of two (shifts) are supported. Mod and Rem are not supported in MAX+PLUS II. Efficient design of multiply or divide hardware typically requires the user to specify the arithmetic algorithm and design in VHDL.
** Supported only in 1076-1993 VHDL.

Note:
VHDL is not case sensitive

Concurrent and Sequential Statements

- **Concurrent statements**
 - Signal assignment
 - Conditional signal assignment (WHEN-ELSE)
 - Selected signal assignment (WITH-SELECT-WHEN)
 - Process
- **Statements inside a process are executed sequentially**
 - Variables, arrays, queues
 - Variable assignments (no delay)
 - IF-THEN-ELSE, CASE-WHEN, LOOP
 - WAIT UNTIL, WAIT FOR, WAIT ON
 - *WARNING — not everything you do in a process may be synthesizable by your synthesis tools!*

11

Spring 2006, Lecture 18

Four Multiplexers

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY multiplexer IS
    PORT( A, B, Mux_Control : IN  STD_LOGIC;
          Mux_Out1, Mux_Out2,
          Mux_Out3, Mux_Out4 : OUT STD_LOGIC );
END multiplexer;

ARCHITECTURE behavior OF multiplexer IS
BEGIN
    -- selected signal assignment statement/
    Mux_Out1 <= A WHEN Mux_Control = '0' ELSE B;
    -- / with Select Statement


    WITH mux_control SELECT

    Mux_Out2 <=  A WHEN '0',
                 B WHEN '1',
                 A WHEN OTHERS;
    -- OTHERS case required since STD_LOGIC
    -- has values other than "0" or "1"

    PROCESS ( A, B, Mux_Control )
    BEGIN
        -- Statements inside a process
        -- execute sequentially.
        IF Mux_Control = '0' THEN
            Mux_Out3 <= A;
        ELSE
            Mux_Out3 <= B;
        END IF;

        CASE Mux_Control IS
            WHEN '0' =>
                Mux_Out4 <= A;
            WHEN '1' =>
                Mux_Out4 <= B;
            WHEN OTHERS =>
                Mux_Out4 <= A;
        END CASE;
    END PROCESS;
END behavior;

```

 

12

Spring 2006, Lecture 18

Signal Assignment

■ Concurrent signal assignment

- Example: `a <= '1'; z <= a XOR b;`
- LHS signal type must match RHS

■ Conditional signal assignment

- Example: `z <= s0 WHEN sel='0' ELSE s1;`
- Last ELSE should have no condition to handle all cases not otherwise covered

■ Selected signal assignment

- Example: `WITH sel SELECT
z <= s0 WHEN '0', s1 WHEN '1';`
- Cover all cases in mutually-exclusive fashion, possibly use “WHEN OTHERS” for last case

13

Spring 2006, Lecture 18

Processes

■ A process may begin “main: process (A, B)”

- Name of process is “main”
- Sensitivity list for process is “A, B”

■ Sensitivity list

- If one of these signals changes, the process executes
- Should contain any signals on the right-hand-side of an assignment, or in any boolean condition

■ Conditionals in IF statements must return a boolean

- OK to write: `if reset = '1' then...`
- NOT OK to write: `if reset then...`
 - Returns a standard logic type (!)

14

Spring 2006, Lecture 18



Sequential Statements (Inside Process)

■ IF-THEN-ELSE

- Only statements in the first condition matched will be executed
- Nesting allowed, each level adds more multiplexing or other additional logic, so should be done carefully

■ CASE-WHEN

- Good when all branching is based on single condition

■ LOOP, WHILE-LOOP, FOR-LOOP

- Repetition

■ WAIT UNTIL (boolean), WAIT FOR (time expression), WAIT ON (signal) -- waits for event on that signal