

# VHDL Introduction, Part II

Figures in this lecture are from:

*Rapid Prototyping of Digital Systems,  
Second Edition*

James O. Hamblen & Michael D. Furman,  
Kluwer Academic Publishers, 2001,  
ISBN 0-7923-7439-8

**Dr. Robert A. Walker**

Computer Science Department  
Kent State University  
Kent, OH 44242 USA

<http://www.cs.kent.edu/~walker>

## Concurrent & Sequential Stmts. (Review)

### ■ Concurrent statements

- Signal assignment
- Conditional signal assignment (WHEN-ELSE)
- Selected signal assignment (WITH-SELECT-WHEN)
- Process

### ■ Statements inside a process are executed sequentially

- Variables, arrays, queues
- Variable assignments (no delay)
- IF-THEN-ELSE, CASE-WHEN, LOOP
- WAIT UNTIL, WAIT FOR, WAIT ON
- WARNING** — *not everything you do in a process may be synthesizable by your synthesis tools!*


# Four Multiplexers (Review)

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY multiplexer IS
    PORT( A, B, Mux_Control : IN STD_LOGIC;
          Mux_Out1, Mux_Out2,
          Mux_Out3, Mux_Out4 : OUT STD_LOGIC );
END multiplexer;

ARCHITECTURE behavior OF multiplexer IS
BEGIN
    Mux_Out1 <= A WHEN Mux_Control = '0' ELSE B;
    Mux_Out2 <= A WHEN '0',
                B WHEN '1',
                A WHEN OTHERS;
    Mux_Out3 <= A WHEN Mux_Control = '0' THEN
                Mux_Out3 <= A;
                ELSE
                Mux_out3 <= B;
            END IF;
    Mux_Out4 <= A WHEN Mux_Control IS
                WHEN '0' =>
                Mux_Out4 <= A;
                WHEN '1' =>
                Mux_Out4 <= B;
                WHEN OTHERS =>
                Mux_Out4 <= A;
            END CASE;
END PROCESS;
END behavior;
    
```

 

# Four Flip-Flops (Slide 1 of 2)

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;


ENTITY DFFs IS
    PORT( D, Clock, Reset, Enable : IN STD_LOGIC;
          Q1, Q2, Q3, Q4 : OUT STD_LOGIC );
END DFFs;
    
```

```

ARCHITECTURE behavior OF DFFs IS
BEGIN
    
```

```

 PROCESS
BEGIN
    WAIT UNTIL ( Clock 'EVENT AND Clock = '1' );
    Q1 <= D;
END PROCESS;
    
```




## Four Flip-Flops (Slide 2 of 2)

```

PROCESS                               -- Positive edge triggered D flip-flop
BEGIN                                  -- with synchronous reset
    WAIT UNTIL ( Clock 'EVENT AND Clock = '1' );
    IF reset = '1' THEN
        Q2 <= '0';
    ELSE
        Q2 <= D;
    END IF;
END PROCESS;


```

 

```

PROCESS (Reset,Clock)                 -- Positive edge triggered D flip-flop
BEGIN                                  -- with asynchronous reset
    IF reset = '1' THEN
        Q3 <= '0';
    ELSIF ( clock 'EVENT AND clock = '1' ) THEN
        Q3 <= D;
    END IF;
END PROCESS;


```

 

```

PROCESS (Reset,Clock)                 -- Positive edge triggered D flip-flop
BEGIN                                  -- with asynchronous reset and
                                        -- enable
    IF reset = '1' THEN
        Q4 <= '0';
    ELSIF ( clock 'EVENT AND clock = '1' ) THEN
        IF Enable = '1' THEN
            Q4 <= D;
        END IF;
    END IF;
END PROCESS;

```

 

5

END behavior;

Spring 2006, Lecture 19

## Unassigned Outputs => Inferred Latches

- If an output is assigned a value in some paths through an IF or CASE statement, but is unassigned in at least one path, then a latch is added (“inferred”)
- This is a common mistake
  - Make sure ***all*** outputs are assigned a value, no matter what path is taken through the code, or give the signal a default value before the IF or CASE
- If no (new) value is assigned, the synthesis tools will assume you want the old value
  - A latch (register) will be placed on that output
  - Latches add delay, different paths may take different amounts of time, etc.

6

Spring 2006, Lecture 19

## (Accidentally) Inferred Latches


```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY ilatch IS
    PORT( A, B           : IN  STD_LOGIC;
          Output1, Output2 : OUT STD_LOGIC );
END ilatch;

ARCHITECTURE behavior OF ilatch IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = '0' THEN
            Output1 <= '0';
            Output2 <= '0';
        ELSE
            IF B = '1' THEN
                Output1 <= '1';
                Output2 <= '1';
            ELSE
                Output1 <= '0';
            END IF;
        END IF;
    END PROCESS;
END behavior;

```

 *-- Latch inferred since no value is assigned  
-- to output2 in the else clause!*



## 8-Bit Counter

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY Counter IS
    PORT( Clock, Reset : IN  STD_LOGIC;
          Max_count    : IN  STD_LOGIC_VECTOR( 7 DOWNTO 0 );
          Count        : OUT STD_LOGIC_VECTOR( 7 DOWNTO 0 );
END Counter;

ARCHITECTURE behavior OF Counter IS
    SIGNAL internal_count: STD_LOGIC_VECTOR( 7 DOWNTO 0 );
BEGIN
    count <= internal_count;

    PROCESS ( Reset, Clock )
    BEGIN
        IF reset = '1' THEN
            internal_count <= "00000000";
        ELSIF ( clock 'EVENT AND clock = '1' ) THEN
            IF internal_count < Max_count THEN
                internal_count <= internal_count + 1;
            ELSE
                internal_count <= "00000000";
            END IF;
        END IF;
    END PROCESS;
END behavior;

```

*-- Declare signal(s) internal to module*  
*-- Reset counter*  
*-- Check for maximum count*  
*-- Increment Counter*  
*-- Count >= Max\_Count*  
*-- reset Counter*



## ALU with Shifter (Slide 1 of 2)

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY ALU IS
    PORT( Op_code           : IN  STD_LOGIC_VECTOR( 2 DOWNTO 0 );
          A_input, B_input  : IN  STD_LOGIC_VECTOR( 7 DOWNTO 0 );
          ALU_output        : OUT STD_LOGIC_VECTOR( 7 DOWNTO 0 );
    END ALU;

    ARCHITECTURE behavior OF ALU IS
        -- Declare signal(s) internal to module here
        SIGNAL temp_output  : STD_LOGIC_VECTOR( 7 DOWNTO 0 );
    BEGIN

        PROCESS ( Op_code, A_input, B_input )
            BEGIN
```

9

Spring 2006, Lecture 19




## ALU with Shifter (Slide 2 of 2)

```
    CASE Op_Code ( 2 DOWNTO 1 ) IS -- Select Arithmetic/Logical Operation
        WHEN "00" =>
            temp_output <= A_input + B_input;
        WHEN "01" =>
            temp_output <= A_input - B_input;
        WHEN "10" =>
            temp_output <= A_input AND B_input;
        WHEN "11" =>
            temp_output <= A_input OR B_input;
        WHEN OTHERS =>
            temp_output <= "00000000";
    END CASE;

    -- Select Shift Operation: Shift bits left with zero fill using concatenation operator
    -- Can also use VHDL 1076-1993 shift operator such as SLL

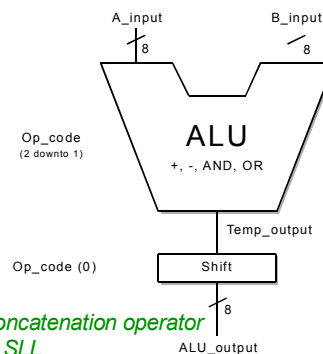    IF Op_Code( 0 ) = '1' THEN
        Alu_output <= temp_output( 6 DOWNTO 0 ) & '0';
    ELSE
        Alu_output <= temp_output;
    END IF;
END PROCESS;
END behavior;
```



10

Spring 2006, Lecture 19



## State Machine Example (Slide 1 of 2)

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
  
ENTITY st_mach IS  
    PORT( clk, reset      : IN    STD_LOGIC;  
          Input1, Input2  : IN    STD_LOGIC;  
          Output1         : OUT   STD_LOGIC);  
END st_mach;
```

```
ARCHITECTURE A OF st_mach IS
```

*-- Enumerated Data Type for State*

```
    TYPE STATE_TYPE IS ( state_A, state_B, state_C );  
    SIGNAL state: STATE_TYPE;
```

```
BEGIN
```


```
    PROCESS ( reset, clk )
```

```
    BEGIN
```

```
        IF reset = '1' THEN -- Reset State
```

```
            state <= state_A;
```
 
```
        ELSIF clk 'EVENT AND clk = '1' THEN
```



## State Machine Example (Slide 2 of 2)

```
CASE state IS -- Define Next State Transitions using a Case  
    -- Statement based on the Current State
```

```
    WHEN state_A =>  
        IF Input1 = '0' THEN  
            state <= state_B;  
        ELSE  
            state <= state_C;  
        END IF;
```

```
    WHEN state_B =>  
        state <= state_C;
```

```
    WHEN state_C =>  
        IF Input2 = '1' THEN  
            state <= state_A;  
        END IF;
```

```
    WHEN OTHERS =>  
        state <= state_A;
```

```
END CASE;
```

```
END IF;
```

```
END PROCESS;
```

```
WITH state SELECT
```

```
    Output1 <= '0' WHEN state_A,  
              '1' WHEN state_B,  
              '0' WHEN state_C;
```

*-- Define State Machine Outputs*

```
END a;
```

