

Due to Prof. Walker by 5:30pm on Wednesday 15 March 2006
this project counts as 10% of your course grade

1. Review the design of the 3-bit counter using D flip-flops in the attached handout. Implement this counter using the FLEX chip on the UP1 board, with the output of the counter displayed on a 7-segment LED, such that the circuit counts to the next value each time a pushbutton is pressed. Turn in:
 - a) a description of your design and any design decisions that you made in your implementation (15 points)
 - b) a readable (not microscopic) printout of the schematic (5 points)
 - c) a printout of the test inputs and simulation output that shows that that the circuit works as expected, annotated to explain the operation of the circuit (15 points)
 - d) a signature on the statement below by Prof. Walker, by the TA (Kevin Schaffer), by one of Prof. Walker's research students listed on the door of the lab, or by two other students in the class (15 points):

I certify that _____ has successfully downloaded this design to a UP1 board and the design works correctly.

_____ Name _____ Date

_____ Name _____ Date

2. Design a 3-bit counter, implemented on the FLEX chip using the 7-segment LED and pushbutton as in Problem 1, but instead of entering the counter graphically, enter it using AHDL design in a style to the one on page 162 of *Digital Systems Design and Prototyping*. Turn in:
 - a) items (a) through (c) similar to those in problem 1 above (35 points)
 - b) a signature on the statement below by Prof. Walker, by the TA (Kevin Schaffer), by one of Prof. Walker's research students listed on the door of the lab, or by two other students in the class (15 points):

I certify that _____ has successfully downloaded this design to a UP1 board and the design works correctly.

_____ Name _____ Date

_____ Name _____ Date